

Fondamenti di Elettronica - Ingegneria Elettronica – a.a. 2011/12

Midterm Examination – May 3th, 2012

State clearly the question you are answering. E.g. 1a).
Solve first questions in bold. This is a 3-hour in-class closed-book exam.

EXERCISE 0 –BOLD QUESTIONS MANDATORY (otherwise all the other exercises will not be corrected).

Consider the circuit shown in Fig. 1a.

- a) Find the average value of the voltage V_{out} when the input voltage is a sinusoidal signal with amplitude equal to $1V$ and frequency $1kHz$.**
- b) Draw in a time diagram, providing values for all the relevant points, the curve of the voltage $V_{out}(t)$, when the input current is the one shown in Fig. 1b (*non-periodic*). Provide justification for your answer.

 


Fig. 1a

Fig. 1b

Exercise 1

Let's refer to the MOSFET circuit shown in Fig. 2. v_{in} is a small signal voltage generator.

- a) Find the value of resistor R_s that guarantees a bias current of $1mA$ flowing in the MOSFET. Find, then, the DC voltages at all nodes and the DC current in all branches**
- b) Find the small-signal voltage gain $v_{out,2}/v_{in}$ at high frequency (i.e. consider all capacitances as short circuits).**
- c) Find the small-signal voltage gain $v_{out,1}/v_{in}$ at low frequency (i.e. consider all capacitances as open circuits), assuming that the transistor features an output resistance $r_0 = 100k\Omega$.
- d) Find the singularities introduced by the capacitors C_1 and C_2 in the transfer function $v_{out,1}/v_{in}$, assuming that the transistor features an output resistance $r_0 = \infty$.

 


Fig. 2

$$\begin{aligned} \frac{1}{2}\mu_n C_{ox} &= 50 \mu A/V^2 & (W/L)_n &= 5 & V_{Tn} &= 0.8V \\ R_{in} &= 5k\Omega & R_2 &= 500\Omega & C_2 &= 700pF \\ R_d &= 5k\Omega & R_1 &= 10k\Omega & C_1 &= 50pF \\ V^+ &= +6V & V^- &= -6V \end{aligned}$$

Exercise 2

Let's consider the CMOS logic gate shown in Fig. 3, that implements the logic function $Y = \overline{(A+B) \cdot (C+D \cdot E)} \cdot A$.

- a) Implement the logic function in conventional CMOS technology in its minimal form, drawing the pull-up and the pull-down networks and justifying all the choices.**
- b) Compute the propagation delay of the gate, when all the inputs are short circuited and driven by a single logic signal.
- c) Compute if the logic gate obtained when all the inputs are short circuited and driven by a 50% duty-cycle, $200MHz$ frequency logic signal can properly switch. Justify your answer.

 


Fig. 3

$$\begin{aligned} k_n &= \frac{1}{2} \cdot \mu_n C_{ox} (W/L)_n = 100 \mu A/V^2 \\ |k_p| &= \frac{1}{2} \cdot \mu_p C_{ox} (W/L)_p = 200 \mu A/V^2 \\ |V_{Tp}| &= V_{Tn} = 0.5V & C_L &= 3 pF \end{aligned}$$

Exercise 3

Let us consider the circuit shown in Fig. 4. The diodes D_1 and D_2 are on when forward biased with $0.7V$. The voltage V_{in} is a saw-tooth signal with period $T = 10ms$, peak-to-peak amplitude equal to $8V$ and zero mean value.

- a) Draw in a time diagram, providing values for all the relevant points, the curve of the voltage $V_{out}(t)$.**
- b) If diode D_1 features a break-down voltage $V_{BD} = -5V$, draw in a time diagram, providing values for all the relevant points, the curve of the voltage $V_{out}(t)$.

 


Fig. 4

$$\begin{aligned} V^+ &= 4V \\ V^- &= -2V \\ I &= 100\mu A \\ R_1 &= 1k\Omega \\ R_2 &= 2k\Omega \end{aligned}$$

This document was created with Win2PDF available at <http://www.win2pdf.com>.
The unregistered version of Win2PDF is for evaluation or non-commercial use only.
This page will not be added after purchasing Win2PDF.