



**Fondamenti di Elettronica - Ingegneria Elettronica – a.a. 2009/10**  
**Midterm Examination – May 6<sup>th</sup>, 2010**

State clearly the question you are answering. E.g. 1a).  
 Solve first questions in bold. This is a 3-hour in-class closed-book exam.

**EXERCISE 0 –MANDATORY (otherwise all the other exercises will not be corrected).**

Consider the circuit shown in Fig. 1a.

  - a) **Find the average value of the current  $I_{out}$  when the input current is the one shown in Fig. 1b.**
- b) **Draw in a time diagram, providing values for all the relevant points, the curve of the voltage  $V_{out}(t)$ , when the input current is the one shown in Fig. 1b. Provide justification for your answer.**

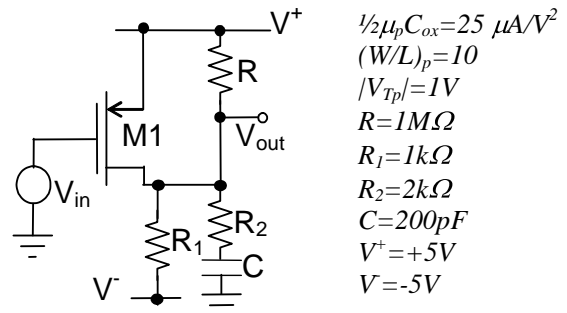


**Fig. 1b**  
 $R_1 = 3k\Omega$                        $R_2 = 1k\Omega$   
 $C = 100pF$   
 $V_+ = +5V$                        $V_- = -4V$

**Exercise 1**

Let's refer to the MOSFET circuit shown in Fig. 2.

- a) **Find the DC voltages at all nodes and the DC current in all branches.**
- b) **Find the small-signal voltage gain  $v_{out}/v_{in}$  at low frequency ( $C$  open circuit).**
- c) Find the singularities introduced by the capacitor  $C$  in the transfer function  $v_{out}/v_{in}$ .
- d) Determine the maximum value of the resistor  $R_1$  that allows "proper operation" of the circuit, considering the behavior at low frequency ( $C$  open circuit).




**Fig. 2**

$\frac{1}{2}\mu_p C_{ox} = 25 \mu A/V^2$   
 $(W/L)_p = 10$   
 $|V_{Tp}| = 1V$   
 $R = 1M\Omega$   
 $R_1 = 1k\Omega$   
 $R_2 = 2k\Omega$   
 $C = 200pF$   
 $V^+ = +5V$   
 $V^- = -5V$

**Exercise 2**

Let's consider the CMOS logic gate shown in Fig. 3, that implements the logic function  $Y = \overline{A \cdot (B + C + A) \cdot D \cdot E}$ .

- a) **Implement the logic function in conventional CMOS technology in its minimal form, drawing the pull-up and the pull-down networks and justifying all the choices.**
- b) Find the combination of the inputs that determines the fastest *LH* and *HL* transitions and compute those transition times.
- c) Compute the power dissipated by the logic gate if inputs *B* and *C* are both driven by a clock signal with *1 MHz* frequency, input *A* is kept high and inputs *D* and *E* are kept low.

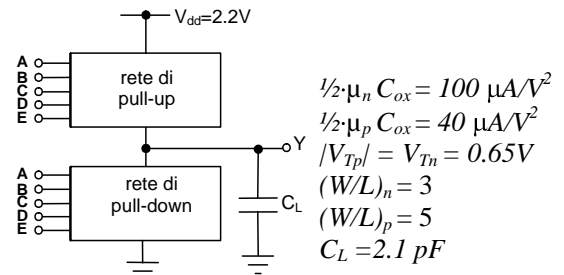


**Fig. 3**

$\frac{1}{2}\mu_n C_{ox} = 100 \mu A/V^2$   
 $\frac{1}{2}\mu_p C_{ox} = 40 \mu A/V^2$   
 $|V_{Tp}| = V_{Tn} = 0.65V$   
 $(W/L)_n = 3$   
 $(W/L)_p = 5$   
 $C_L = 2.1 pF$

**Exercise 3**

Let us consider the circuit shown in Fig. 4. The diode *D* is on when forward biased with *0.7 V*. The voltage  $V_{in}$  is a sinusoidal signal with frequency  $f = 5 kHz$  and amplitude  $A = 5 V$ .

- a) **Draw in a time diagram, providing values for all the relevant points, the curve of the current  $I_{out}(t)$ .**
- b) If the diode features a break-down voltage  $|V_{BD}| = 5V$ , draw in a time diagram, providing values for all the relevant points, the curve of the power dissipated by the diode.

 

**Fig. 4**

$R_1 = 1 k\Omega$                        $R_2 = 2k\Omega$