

Fondamenti di Elettronica - Ingegneria Elettronica – a.a. 2014/15

Unscheduled Examination – May 7th, 2015

State clearly the question you are answering. E.g. 1a).
Solve first questions in bold. This is a 3-hour in-class closed-book exam.

Exercise 1

Let's consider again the circuit shown in Fig. 1a.

- Draw in a time diagram, providing values for all the relevant points, the curve of the current $I_{out}(t)$, when the input voltage is the one shown in Fig. 1b (periodic), if $T = 48\text{ ms}$. Provide justification for your answer.
- Draw in a time diagram, providing values for all the relevant points, the curve of the voltage $V_{out}(t)$, when the input voltage is the one shown in Fig. 1b (periodic), if $T = 2.4\text{ ms}$. Provide justification for your answer.

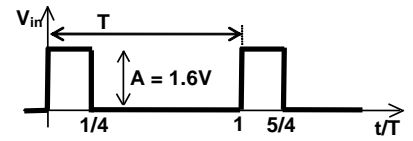
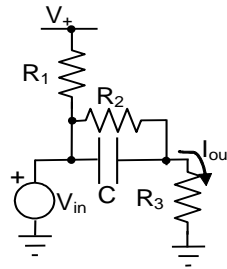


Fig. 1b
 $R_1 = 1\text{ k}\Omega$

$$R_2 = 3\text{ k}\Omega \quad R_3 = 4\text{ k}\Omega$$

$$C = 200\text{ nF} \quad V_+ = +3\text{ V}$$

Fig. 1a

Exercise 2

Let's refer to the MOSFET circuit shown in Fig. 2. i_{in} is a small signal current generator.

- Find the value of resistor R_s that provides 1 mA static current in the transistor. Find, then, the circuit bias point (i.e. the DC voltages at all the nodes and the DC current in all the branches).
- Find the small-signal transfer function v_{out}/i_{in} at high frequency (C_1 e C_2 short-circuited).
- Draw the magnitude Bode diagram of the transfer function v_{out}/i_{in} .
- Find the maximum current amplitude, in the case of a sinusoidal signal at 5 Hz frequency, that ensures a linearity error below or equal to 4%.

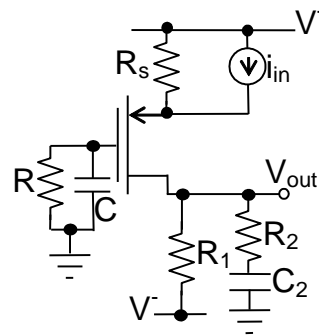


Fig. 2

$$V_+ = -V = 4\text{ V}$$

$$|k_p| = \frac{1}{2} \mu_p C_{ox} (W/L)_p = 1\text{ mA/V}^2$$

$$V_{Tp} = -1\text{ V}$$

$$R = 2.5\text{ M}\Omega$$

$$R_1 = 4\text{ k}\Omega$$

$$C = 220\text{ nF}$$


$$C_2 = 47\text{ nF}$$

$$R_2 = 4\text{ k}\Omega$$

$$r_0 = \infty$$

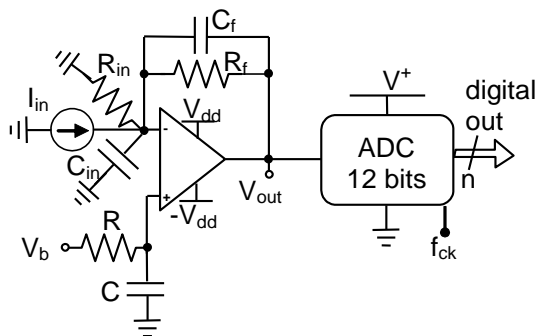Exercise 3

Let's consider the acquisition chain shown in Fig. 3. Let us assume that the operational amplifier saturates at the power supply voltages. The ADC is based on a successive approximation logic.



$$V^+ = 2.5\text{ V}$$

$$V_{dd} = 5\text{ V}$$

$$R_{in} = 100\text{ k}\Omega$$

$$R_f = 10\text{ M}\Omega$$

$$R = 10\text{ k}\Omega$$

$$C = 1\text{ }\mu\text{F}$$

$$C_f = 2\text{ pF}$$

$$C_{in} = 5\text{ pF}$$

$$f_{ck} = 5\text{ MHz}$$

- Draw the magnitude Bode diagram of the transfer function V_{out}/I_{in} assuming an ideal operational amplifier and $V_b = 0\text{ V}$.
- Find the achievable input resolution when converting a zero-average sinusoidal current with 100 nA amplitude and 100 Hz frequency and the required value for the voltage V_b .
- Find the maximum frequency of a sinusoidal current signal with maximum amplitude compatible with the ADC dynamic range (assume the proper value of V_b is given) that can be properly digitized with an error below or equal to 1 LSB .
- Draw the magnitude Bode diagram of the transfer function V_{out}/I_{in} if the operational amplifier feature a gain-bandwidth product $GBWP = 5\text{ MHz}$, assuming $V_b = 0\text{ V}$.