

**Fondamenti di Elettronica - Ingegneria Elettronica – a.a. 2014/15**  
**Midterm Examination – May 7<sup>th</sup>, 2015**

State clearly the question you are answering. E.g. 1a). Solve first questions in bold.  
 Solve first questions in bold. This is a 3-hour in-class closed-book exam

**EXERCISE 0 – MANDATORY**

**(otherwise all the other exercises will not be corrected).**

Consider the circuit shown in Fig. 1a.

Find the circuit time constant and the average value of the output current  $I_{out}$ , when the input voltage is the signal shown in Fig. 1b (periodic), if  $T = 48\text{ ms}$ .

 


Fig. 1a

$R_1 = 1\text{ k}\Omega$   
 $R_2 = 3\text{ k}\Omega$   
 $R_3 = 4\text{ k}\Omega$   
 $C = 200\text{ nF}$   
 $V_+ = +3\text{ V}$

 


Fig. 1b

**Exercise 1**

Let's consider again the circuit shown in Fig. 1a.

- Draw in a time diagram, providing values for all the relevant points, the curve of the current  $I_{out}(t)$ , when the input voltage is the one shown in Fig. 1b (periodic), if  $T = 48\text{ ms}$ . Provide justification for your answer.
- Draw in a time diagram, providing values for all the relevant points, the curve of the voltage  $I_{out}(t)$ , when the input voltage is the one shown in Fig. 1b (periodic), if  $T = 2.4\text{ ms}$ . Provide justification for your answer.

**Exercise 2**

Let's refer to the MOSFET circuit shown in Fig. 2.  $i_{in}$  is a small signal current generator.

- Find the value of resistor  $R_s$  that provides  $1\text{ mA}$  static current in the transistor. Find, then, the circuit bias point (i.e. the DC voltages at all the nodes and the DC current in all the branches).
- Find the small-signal transfer function  $v_{out}/i_{in}$  at high frequency ( $C$  e  $C_2$  short-circuited).
- Find the singularities introduced by capacitors  $C$  e  $C_2$  in the transfer function  $v_{out}/i_{in}$ .
- Find the maximum current amplitude, in the case of a sinusoidal signal at  $5\text{ Hz}$  frequency, that ensures a linearity error below or equal to 4%.

 


Fig. 2

$V_+ = -V = 4\text{ V}$   
 $|k_p| = 1/2 \mu_p C_{ox} (W/L)_p = 1\text{ mA/V}^2$   
 $V_{Tp} = -1\text{ V}$   
 $R = 2.5\text{ M}\Omega$   
 $R_1 = 4\text{ k}\Omega$   
 $C = 220\text{ nF}$   
 $C_2 = 47\text{ nF}$   
 $R_2 = 4\text{ k}\Omega$   
 $r_0 = \infty$

**Exercise 3**

Let's consider the CMOS logic gate shown in Fig. 3, that implements the logic function  $Y = \overline{(A+B)} \cdot \overline{(C+D)} + \overline{A} \cdot \overline{B}$ .

- Implement the logic function in conventional CMOS technology in its minimal form, drawing the pull-up and the pull-down networks and justifying all the choices.
- Find the maximum time interval, following an low-high output switch, during which the transistors that switch on are biased in the saturation region.

 


Fig. 3

$k_n = 1/2 \mu_n C_{ox} (W/L)_n = 200\text{ }\mu\text{A/V}^2$   
 $|k_p| = 1/2 \mu_p C_{ox} (W/L)_p = 60\text{ }\mu\text{A/V}^2$   
 $|V_{Tp}| = V_{Tn} = 0.65\text{ V}$   
 $C_L = 650\text{ fF}$

**Exercise 4**

Let us consider the circuit shown in Fig. 4a. The diode is on when forward biased with  $0.7\text{ V}$  and operates in the breakdown region if the reverse voltage overcomes  $4.7\text{ V}$ .

Draw the transfer characteristics  $V_{out}$  vs.  $V_{in}$ , quoting all the relevant points and providing adequate justification for your answer, assuming that the input current varies in the interval  $[-2\text{ mA}; 2\text{ mA}]$ .

 


Fig. 4a

$V_+ = 3\text{ V}$   
 $R_1 = 1\text{ k}\Omega$   
 $R_2 = 3\text{ k}\Omega$   
 $R_3 = 2\text{ k}\Omega$   
 $R_4 = 4\text{ k}\Omega$