

Fondamenti di Elettronica - Ingegneria Elettronica – a.a. 2012/13

Unscheduled Examination – May 10th, 2013

State clearly the question you are answering. E.g. 1a). Solve first questions in bold.
Solve first questions in bold. This is a 3-hour in-class closed-book exam.

Exercise 1

Let's consider the circuit shown in Fig. 1a.

- a) **Draw in a time diagram, providing values for all the relevant points, the curve of the voltage $V_{out}(t)$, when the input current is the one shown in Fig. 1b (non-periodic). Provide justification for your answer.**

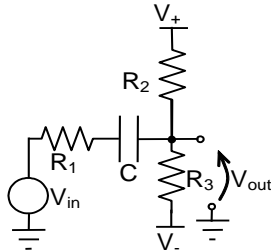


Fig. 1a

$$\begin{aligned} R_1 &= 3k\Omega \\ R_2 &= 3k\Omega \\ R_3 &= 1k\Omega \\ C &= 1nF \\ V_- &= -2V \\ V_+ &= +2V \end{aligned}$$

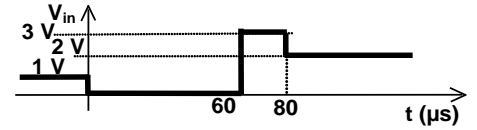


Fig. 1b

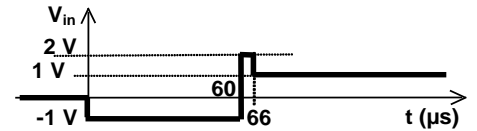


Fig. 1c

- b) Draw in a time diagram, providing values for all the relevant points, the curve of the voltage $V_{out}(t)$, when the input current is the one shown in Fig. 1c (non-periodic). Provide justification for your answer.

Exercise 2

Let's refer to the MOSFET circuit shown in Fig. 2. v_{in} is a small signal voltage generator.

- Find the value of the form factor $(W/L)_2$ of transistor M2 that guarantees a bias current of 1 mA flowing in M2. Find, then, the DC voltages at all the nodes and the DC current in all the branches
- Find the small-signal voltage gain $v_{out,2}/v_{in}$ at low frequency (i.e. consider C as open circuit).
- Draw the magnitude Bode diagram of the small signal voltage transfer v_{out}/v_{in} .
- Find the maximum allowed value for resistor R_d that guarantees that both transistors are operating in saturation.

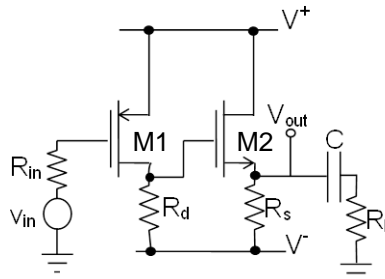


Fig.2

$$\begin{aligned} \frac{1}{2}\mu_n C_{ox} &= 100 \mu A/V^2 \\ |k_p| &= \frac{1}{2}\mu_p C_{ox} (W/L)_p = 100 \mu A/V^2 \\ V_{Tn} &= |V_{Tp}| = 1V \\ R_{in} &= 50\Omega \\ R_s &= 900\Omega \\ C &= 47nF \\ R_d &= 3k\Omega \\ R_L &= 10k\Omega \\ V^+ &= +5V \\ V^- &= -5V \\ r_o &= \infty \end{aligned}$$

Exercise 3

Let us consider the data acquisition system shown in Fig. 3. Let us assume that the operational amplifier saturates at the power supply voltages.

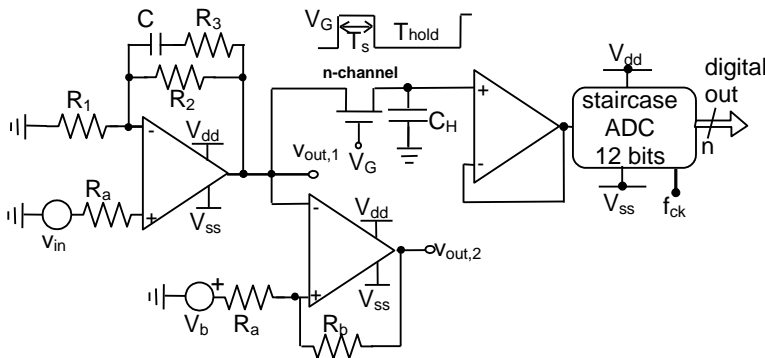


Fig. 3

- Draw the diagram of the input-output transfer characteristics ($v_{out,2}/v_{out,1}$), quoting all the relevant points and showing the reasoning performed to compute the behaviour of the transfer characteristics.
- Draw the magnitude Bode diagram of the transfer function $V_{out,1}/V_{in}$, quoting all the relevant points.
- Let's consider a DC input voltage equal to -100mV. Find the limiting values of the drive voltage to be applied to the gate of the MOS transistor able to guarantee an ideally infinite resistance $R_{ds,off}$ during the Hold phase and a resistance $R_{ds,on}$ below 8 Ω in the Sample phase.
- Determine the minimum value of the Hold capacitor (C_H) that guarantees that a droop rate below $\frac{1}{2}$ LSB/ms, if the opamp used for the buffer features a differential input resistance $R_{id} = 10 M\Omega$ and an open loop gain $A_0 = 70dB$.
- Find the minimum value of the ADC clock frequency needed to properly sample a 10 kHz input sinusoidal signal, if the ADC is based on the staircase working principle (Let's assume a duration of the Sample Phase equal to the clock period).

$$\begin{aligned} C &= 47pF \\ R_1 &= 1k\Omega \\ R_2 &= 19k\Omega \\ R_3 &= 10k\Omega \\ R_a &= 2k\Omega \\ R_b &= 3k\Omega \\ V_{dd} &= +5V \\ V_{ss} &= -5V \\ k_n &= \frac{1}{2}\mu_n C_{ox} (W/L)_n = 5 mA/V^2 \\ V_{Tn} &= 1V \end{aligned}$$