

# Fondamenti di Elettronica - Ingegneria Elettronica – a.a. 2012/13

## Midterm Examination – May 10<sup>th</sup>, 2013

State clearly the question you are answering. E.g. 1a). Solve first questions in bold.  
Solve first questions in bold. This is a 3-hour in-class closed-book exam.

### EXERCISE 0 – BOLD QUESTIONS MANDATORY

(otherwise all the other exercises will not be corrected).

Consider the circuit shown in Fig. 1a.

**Find the circuit time constant and the asymptotic values of the output voltage  $V_{out}$ , for  $t$  tending to  $+\infty$  and to  $-\infty$ , when the input voltage is the signal shown in Fig. 1b.**

 


Fig. 1°

- $R_1 = 3k\Omega$
- $R_2 = 3k\Omega$
- $R_3 = 1k\Omega$
- $C = 1nF$
- $V_- = -1V$
- $V_+ = +3V$

 


Fig. 1b

### Exercise 1

Let's consider again the circuit shown in Fig. 1a.

- a) Draw in a time diagram, providing values for all the relevant points, the curve of the voltage  $V_{out}(t)$ , when the input current is the one shown in Fig. 1b (*non-periodic*). Provide justification for your answer.
- b) Draw in a time diagram, providing values for all the relevant points, the curve of the voltage  $V_{out}(t)$ , when the input current is the one shown in Fig. 1c (*non-periodic*). Provide justification for your answer.

 


Fig. 1c

### Exercise 2

Let's refer to the MOSFET circuit shown in Fig. 2.  $v_{in}$  is a small signal voltage generator.

- a) **Find the value of the form factor  $(W/L)_2$  of transistor M2 that guarantees a bias current of 1 mA flowing in M2. Find, then, the DC voltages at all the nodes and the DC current in all the branches**
- b) **Find the small-signal voltage gain  $v_{out,2}/v_{in}$  at low frequency (i.e. consider C as open circuit).**
- c) Find the singularities introduced by capacitors C in the transfer function  $v_{out}/v_{in}$ .
- d) Find the maximum allowed value for resistor  $R_d$  that guarantees that both transistors are operating in saturation.

 


Fig. 2

- $\frac{1}{2}\mu_n C_{ox} = 100 \mu A/V^2$
- $|k_p| = \frac{1}{2}\mu_p C_{ox} (W/L)_p = 100 \mu A/V^2$
- $V_{Tn} = |V_{Tp}| = 1V$
- $R_{in} = 50\Omega$
- $R_s = 900\Omega$
- $C = 47nF$
- $R_d = 3k\Omega$
- $R_L = 10k\Omega$
- $V^+ = +5V$
- $V^- = -5V$
- $r_0 = \infty$

### Esercizio 3

Let's consider the CMOS logic gate shown in Fig. 3, that implements the logic function  $Y = [A \cdot (B + C)] \cdot A \cdot D$ .

- a) **Implement the logic function in conventional CMOS technology in its minimal form, drawing the pull-up and the pull-down networks and justifying all the choices.**
- b) Determine the transition featuring the shortest transition time and compute such transition time.

 


Fig. 3

- $k_n = \frac{1}{2} \cdot \mu_n C_{ox} (W/L)_n = 100 \mu A/V^2$
- $|k_p| = \frac{1}{2} \cdot \mu_p C_{ox} (W/L)_p = 40 \mu A/V^2$
- $|V_{Tp}| = V_{Tn} = 0.7V$
- $C_L = 20 pF$

### Exercise 4

Let us consider the circuit shown in Fig. 4. The diodes  $D_1$  and  $D_2$  are on when forward biased with 0.7 V. The voltage  $V_{in}$  varies in the range  $[-10V, +10V]$ .

- a) **Draw the input-output transfer curve ( $V_{out}(t)$  vs.  $V_{in}(t)$ ), providing justification for your answer.**
- b) Find the minimum value of the break-down voltage that diode  $D_2$  should feature to avoid its operation in the break-down region.

 


Fig. 4

- $V^+ = 10V$
- $V^- = -10V$
- $R_1 = 20 k\Omega$
- $R_2 = 10 k\Omega$
- $R_3 = 20 k\Omega$