 


Fondamenti di Elettronica - Ingegneria Elettronica – a.a. 2009/10
2nd Examination – September 13th, 2010

State clearly the question you are answering. E.g. 1a).
 Solve first questions in bold. This is a 3-hour in-class closed-book exam.

Exercise 1

Let us consider the circuit for the amplification and the conversion of signals shown in Fig. 1. The ADC is of the staircase type and features n bits.



$$R = 10 \text{ k}\Omega$$

$$|V_{Tp}| = 0.8 \text{ V}$$

$$|k_p| = \frac{1}{2} \mu_p C_{ox} (W/L) = 20 \text{ mA/V}^2$$

$$V_{A+} = |V_{A-}| = 2.5 \text{ V}$$

$$f_{ck} = 30 \text{ MHz}$$

Fig. 1

- Find the maximum number of bits that the ADC can feature in order to properly sample and convert a sinusoidal signal v_{in} with frequency $f = 15 \text{ kHz}$, assuming the minimum sample-time, equal to $1/f_{ck}$. Compute the best resolution that can be guaranteed at the input.**
- Find the voltage V_G to be applied to the gate of the MOSFET switch that guarantees a resistance virtually equal to infinity with 3 V margin during the Hold phase and a resistance not higher than 25Ω during the Sample phase, if the input signal is sinusoidal with amplitude equal to 300 mV .**
- Under the hypothesis that the operational amplifier features a Slew-Rate $SR = 8 \text{ V}/\mu\text{s}$ and the ADC features a number of bits, n , equal to 11, find the maximum sampling frequency that ensures a conversion error lower than 1 LSB, with signals of the maximum dynamics.
- If the operational amplifier has a differential input resistance $R_{id} = 50 \text{ M}\Omega$ and a low frequency open-loop gain $A_0 = 80 \text{ dB}$, find the minimum value of the capacitor C_H that ensures a droop rate lower than 0.5 mV/ms .

Exercise 2

Let us consider the circuit shown in Fig. 2 and assume that the operational amplifiers saturate at the bias voltages.

 


Fig. 2

$$V_{dd} = 3.3 \text{ V}$$

$$R_{in} = 4 \text{ k}\Omega$$

$$R_f = 40 \text{ k}\Omega$$

$$C_f = 2 \text{ pF}$$

$$R_1 = 1 \text{ k}\Omega$$

$$R_2 = 2 \text{ k}\Omega$$

$$R_3 = 0.5 \text{ k}\Omega$$

$$R_4 = 5 \text{ k}\Omega$$

$$C_L = 4 \text{ pF}$$

$$V_{Tn} = |V_{Tp}| = 0.7 \text{ V}$$

$$\frac{1}{2} \mu_p C_{ox} = 30 \text{ }\mu\text{A/V}^2$$

$$(W/L)_p = 20$$

$$\frac{1}{2} \mu_n C_{ox} = 75 \text{ }\mu\text{A/V}^2$$

$$(W/L)_n = 8$$

- Draw the Bode magnitude plot of the transfer function $v_{out,1}/v_{in}$ assuming the operational amplifier ideal and providing values for all the relevant points.**
- Draw the transfer characteristic $v_{out,2}/v_{out,1}$, providing values for all the relevant points.**
- Draw in a time diagram, providing values for all the relevant points, the curve of the voltage $v_{out,3}(t)$, when the output signal of the second operational amplifier, $v_{out,2}$, is a square wave with frequency $f = 10 \text{ MHz}$, keeping into account the propagation times of the inverter.**
- If the first operational amplifier features an open-loop gain $A(s) = A_0/(1+s\tau_0)$, where $A_0 = 80 \text{ dB}$ and $\tau_0 = 15 \text{ ms}$, find the phase margin of the amplifier.
- Find the minimum amplitude of the signal v_{in} that triggers the transition of the output $v_{out,3}$ and find the maximum current flowing from V_{dd} to ground through the transistors during the transition.