
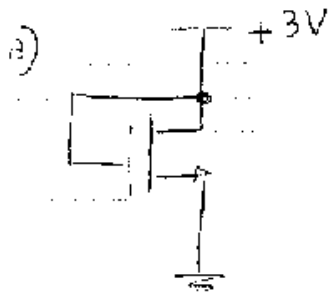


ES. A

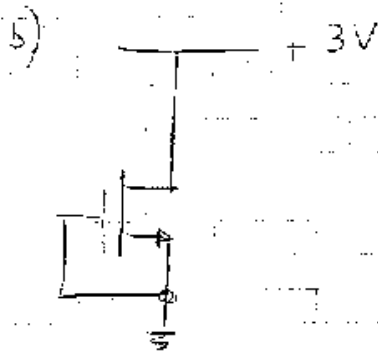

$$\left. \begin{aligned} V_{GS} &= +3V > V_T \\ V_{GD} &= 0V < V_T \end{aligned} \right\} \begin{array}{l} \text{MOS acceso} \\ \text{MOS saturo} \end{array}$$


$$I_D = \beta_n (V_{GS} - V_T)^2 = 1 \text{ mA/V} \cdot (3V - 1V)^2 = 4 \text{ mA}$$




$$\left. \begin{aligned} V_{GD} &= -3V < V_T \\ V_{GS} &= 0V \end{aligned} \right\} \begin{array}{l} \text{MOS spenta} \\ \text{non c' canale} \end{array}$$

$$I_D = 0$$

ES. C

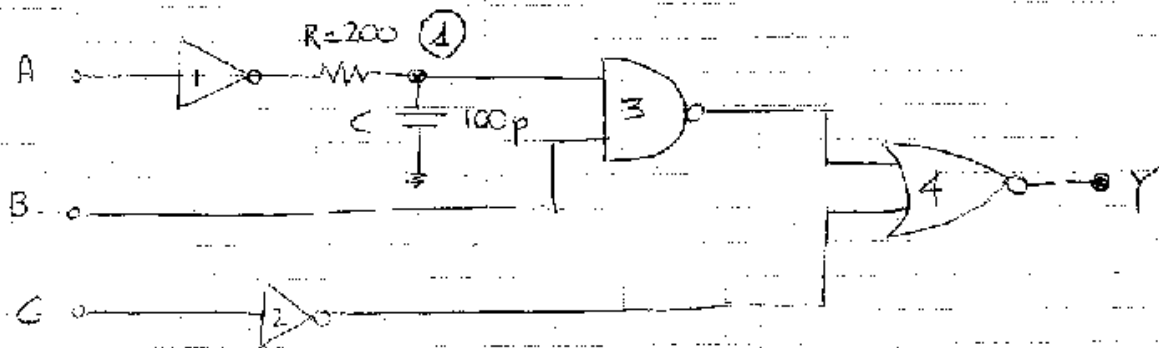

1)	A	B	C	Y	A	B	C	Y
	0	0	0	0	1	1	0	0
	0	0	1	0	1	1	1	0
	0	1	0	0				
	1	0	0	0				
	0	1	1	1				
	1	0	1	0				

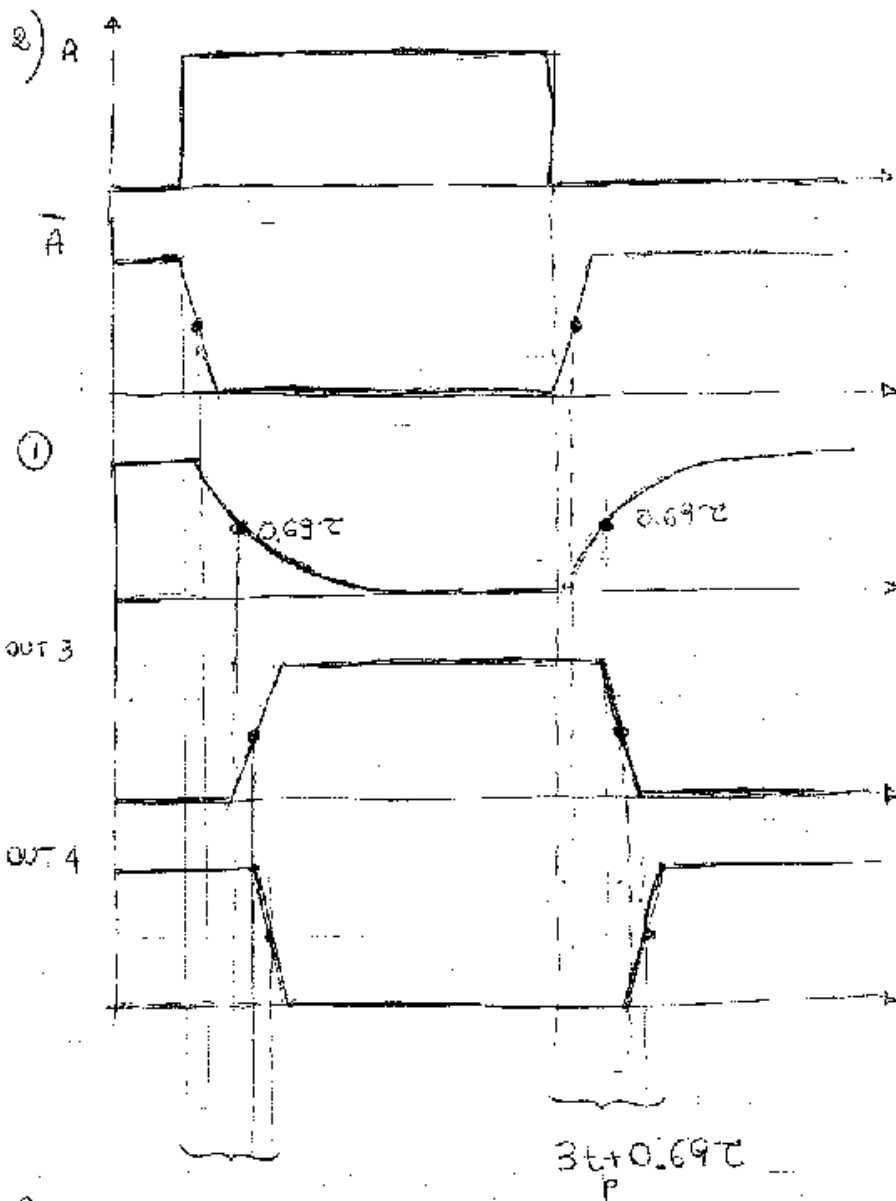

$$\tau = R * C =$$

$$= 200 * 100 \cdot 10^{-12} =$$

$$= 20 \text{ ns}$$

$$t_p = 20 \text{ ns}$$


3) $3t_p + 0.69\tau =$

$$\downarrow$$

$$f_{\text{MAX}} = \left[2 * \left(3t_p + 0.69\tau \right) \right]^{-1} = \left[2 * \left(3 * 20 \text{ ns} + 0.69 * 20 \text{ ns} \right) \right]^{-1} =$$

$$= \left[2 * \left(60 \text{ ns} + 13.8 \text{ ns} \right) \right]^{-1} = \frac{1}{147.6 \text{ ns}} = \underline{6.78 \text{ MHz}}$$

ES. D

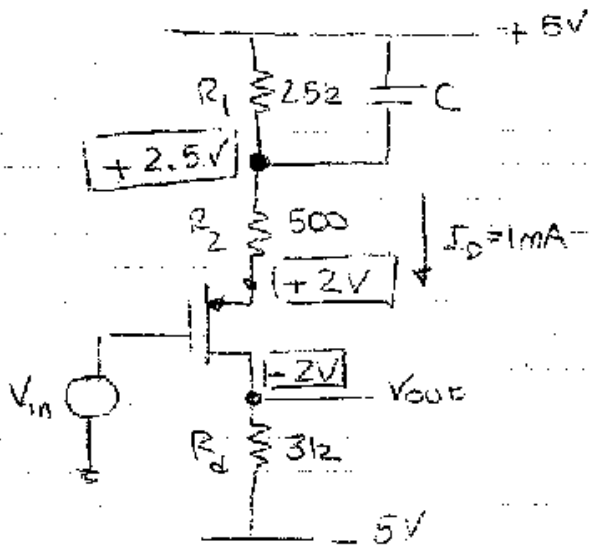

1) $V_{SQ} > 0$

$$\begin{cases} 5V = 3k \cdot I_D + V_{SQ} \\ I_D = k(V_{SQ} - |V_T|)^2 \end{cases}$$

$$5 = 3k \times 1mA / \mu^2 (V_{SQ} - |V_T|)^2 + V_{SQ}$$

$$5 = 3 V_{SQ}^2 = 6 V_{SQ} + 3 \pm V_{SQ}$$

$$3 V_{SQ}^2 - 5 V_{SQ} - 2 = 0$$

$$V_{SQ} = \frac{5 \pm \sqrt{25 + 24}}{6} = \frac{5 \pm 7}{6} \begin{cases} 2V \text{ OK} \\ -2/6 V \text{ No} \end{cases}$$


$$I_D = 1mA / \mu^2 (2V - 1V)^2 = 1mA$$

$$V_{GD} = 2V > V_T \text{ OK}$$

$$g_m = 2k(V_{GS} - V_T) = 2mA/V \Rightarrow \frac{1}{g_m} = 500 \Omega$$



$$2) \left[\frac{v_{out}}{v_{in}} \right]_{LF} = \frac{\frac{1}{g_m}}{\frac{1}{g_m} + R_1 + R_2} (-g_m R_D) = - \frac{g_m R_D}{1 + g_m(R_1 + R_2)} = - \frac{6}{1 + 2 \cdot 3} = - \frac{6}{7} = -0.86$$
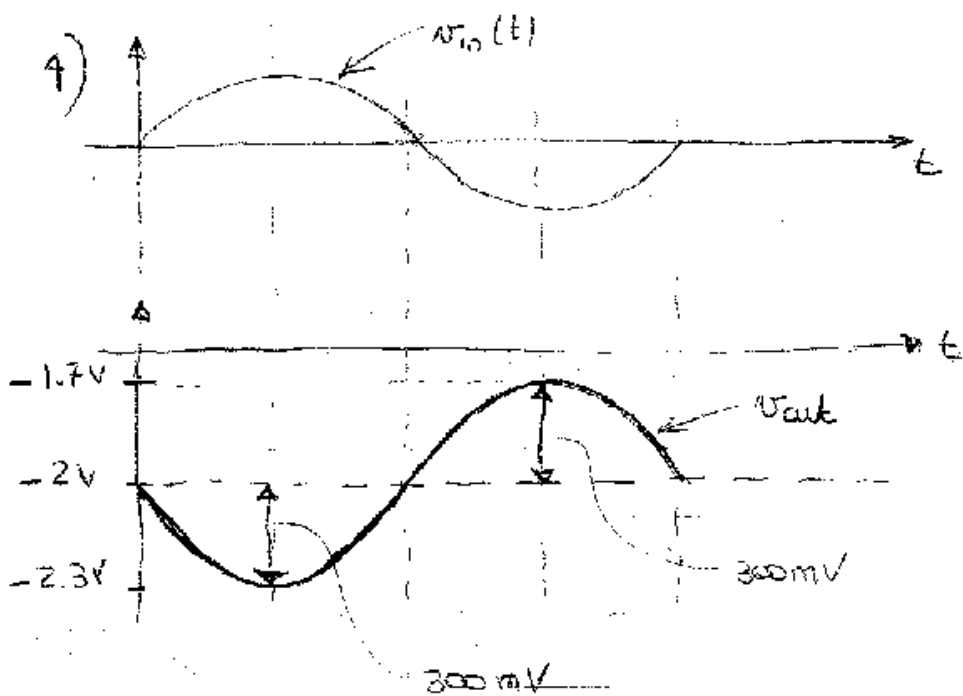
$$3) \left[\frac{v_{out}}{v_{in}} \right]_{HF} = \frac{\frac{1}{g_m}}{\frac{1}{g_m} + R_2} (-g_m R_D) = - \frac{g_m R_D}{1 + g_m R_2} = - \frac{6}{1 + 2 \cdot 0.5} = - \frac{6}{2} = -3$$



ES. B

Semicond. positiva (D_1 e D_3 on)

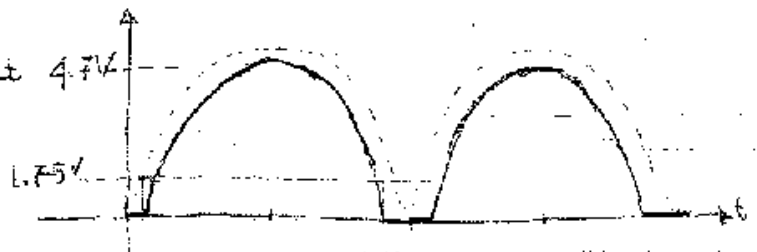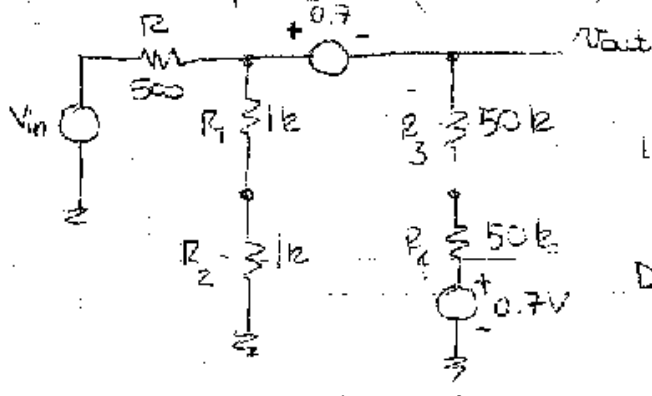

D_1 e D_3 in funcionamento quando:

$$V_{in} + \frac{2\text{k}}{2.5\text{k}} = 1.4\text{V} \Rightarrow V_{in} = 1.4 - \frac{2.5}{2} = 1.75\text{V}$$

al picos:

$$\begin{aligned}
 v_{out} &= 5\text{V} * \frac{(R_3 + R_4) \parallel (R_1 + R_2)}{R + (R_3 + R_4) \parallel (R_1 + R_2)} + 0.7\text{V} \frac{(R_3 + R_4)}{R \parallel (R_1 + R_2) + (R_3 + R_4)} \\
 &+ \frac{R \parallel (R_1 + R_2)}{(R_3 + R_4) \parallel R + (R_3 + R_4)} 0.7\text{V} = 5\text{V} \frac{2\text{k}}{2.5\text{k}} + 0.7\text{V} \frac{100\text{k}}{100\text{k} + \frac{2\text{k} \parallel 500}{400}} \\
 &+ 0.7\text{V} \frac{2\text{k} \parallel 500}{100\text{k} + 2\text{k} \parallel 500} = 5\text{V} \frac{2\text{k}}{2.5\text{k}} + 0.7\text{V} = 4.7\text{V}
 \end{aligned}$$