

Fondamenti di Elettronica - Ingegneria Elettronica -2008/09

Midterm Examination – November 21st, 2008

State clearly the question you are answering. E.g. 1a).
Solve first questions in bold. This is a 3-hour in-class closed-book exam.

Exercise 0 –Mandatory (otherwise all the other exercises will not be corrected).

Consider the circuit shown in Fig. 1a.

Draw in a time diagram, providing values for all the relevant points, the curve of the voltage $V_{out}(t)$ when the input current is the one shown in Fig. 1b.

 


Fig. 1a

 


Fig. 1b

$R_1 = 3k\Omega$ $R_2 = 6k\Omega$
 $C = 220pF$
 $V_1 = -2V$ $V_2 = -1V$

Exercise 1

Again referring to the circuit shown in Fig. 1a.

- Determine the charge stored in the capacitor C when the steady state is reached following the application of the signal shown in Fig. 1b. Provide justification for your answer.**
- How the value of the stored charge in the capacitor C (already calculated in a) would change a long time after the application of the pulse shown in Fig. 1b if the pulse duration would be $1 \mu s$. Provide justification for your answer.

Exercise 2

Let's refer to the *MOSFET* circuit shown in Fig. 2, in which I is a DC current generator.

- Find the DC voltages at all nodes and the DC current in all branches.**
- Find the small-signal voltage gain v_{out}/v_{in} at low frequency (C open circuit).**
- Find the value of the capacitor C that allows the circuit properly amplifying signals in the frequency band [100 Hz, 1.5 MHz].
- How would change the DC bias voltages and currents computed in a) and the small signal gain computed in b) if the current generator I would be a non ideal current generator with an output resistance equal to $120 k\Omega$.

 


Fig. 2

$\frac{1}{2}\mu_p C_{ox} = 20 \mu A/V^2$
 $(W/L)_p = 1$
 $\frac{1}{2}\mu_n C_{ox} = 50 \mu A/V^2$
 $(W/L)_n = 2$
 $V_{Tn} = |V_{Tp}| = 0.5V$
 $R = 20k\Omega$
 $I = 0.2mA$
 $V_{dd} = +3V$
 $V_{ss} = -3V$

Exercise 3

Let's consider the CMOS logic gate shown in Fig. 3, that implements the logic function $Y = \overline{(A \cdot B \cdot C)} + \overline{A} + \overline{D}$.

- Implement the following function in conventional CMOS, drawing the pull-up and the pull-down networks and justifying all the choices.**

Let's suppose to short-circuit all the inputs together and let's consider the equivalent inverter.

- Find the analog voltage range of the output node Y that ensures the operation of the equivalent *pMOSFET* in the saturation region.
- Compute the time needed for the equivalent *pMOSFET* to exit from the saturation region after the transition of the input.

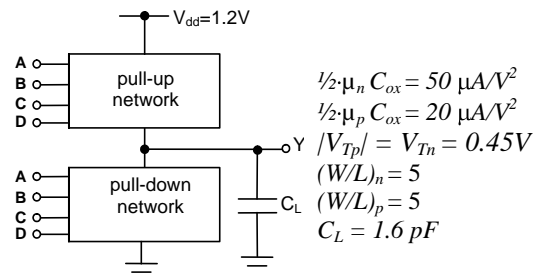


Fig. 3

$\frac{1}{2}\mu_n C_{ox} = 50 \mu A/V^2$
 $\frac{1}{2}\mu_p C_{ox} = 20 \mu A/V^2$
 $|V_{Tp}| = V_{Tn} = 0.45V$
 $(W/L)_n = 5$
 $(W/L)_p = 5$
 $C_L = 1.6 pF$

Exercise 4

Let us consider the circuit shown in Fig. 4. The diodes D_1 and D_2 are on when forward biased with $0.7 V$. The current I_{in} is sinusoidal with frequency $f = 2 kHz$ and amplitude $A = 1 mA$.

Draw in a time diagram, providing values for all the relevant points, the curve of the power dissipated by the diode D_2 .

 


Fig. 4a

$R_1 = 1 k\Omega$ $R_2 = 2k\Omega$ $R_3 = 3k\Omega$

This document was created with Win2PDF available at <http://www.win2pdf.com>.
The unregistered version of Win2PDF is for evaluation or non-commercial use only.