

## TRACCIA DI SOLUZIONE - ESERCIZIO 2

①  $V_G = 4V$ ;  $V_{GS} = 1.68V$ ;  $I_D = 2.32 \text{ mA}$ ;  $V_D = 5.04V$ ;  $V_S = 2.32V$

Il MOSFET è polarizzato in zona di saturazione, infatti  $V_{GD} < V_T$   
 $V_{GS} > V_T$

$g_m = 6.8 \text{ mA/V}$  ;  $1/g_m =$


②  $\frac{V_{out_1}}{V_{in}} = \frac{R_1 \parallel R_2}{R_{in} + R_1 \parallel R_2} \cdot \frac{-g_m R_D}{1 + g_m R_S}$

$R_S \gg 1/g_m$  ( $1 \text{ k}\Omega \gg 147 \Omega$ )  $\Rightarrow \frac{V_{out_1}}{V_{in}} \approx - \frac{R_1 \parallel R_2}{R_{in} + R_1 \parallel R_2} \cdot \frac{R_D}{R_S} =$   
 $= -2.61$

③  $\frac{V_{out_2}}{V_{in}} = \frac{R_1 \parallel R_2}{R_{in} + R_1 \parallel R_2} \cdot \frac{g_m R_S}{1 + g_m R_S} = +0.76$

↳ idealmente guadagna 1: EMITTER FOLLOWER

④ Circuito equivalente visto da (A)

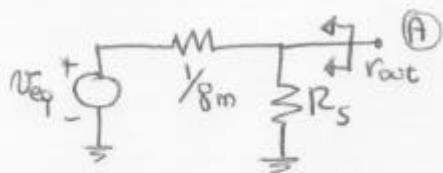

Spegnendo  $V_{eq}$ :

$r_{out} = R_S \parallel 1/g_m \approx 1/g_m = 147 \Omega$

⑤  $P_{TOT} = P_{R_1, R_2} + P_{R_D} + P_{R_S} + P_{MOS} =$

$= V_{DD} \cdot I_{R_1, R_2} + V_{R_D} I_D + V_{R_S} I_D + V_{DS} I_D =$

$= 480 \mu\text{W} + 16.1 \text{ mW} + 5.4 \text{ mW} + 6.31 \text{ mW} \approx 28 \text{ mW}$