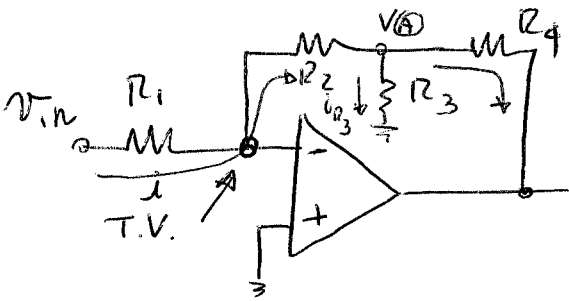


①



$$-v_o / v_i \left( 1 + \frac{R_4}{R_2} + \frac{R_4}{R_3} \right)$$

$$-A_o \left( \frac{R_4}{R_2 + R_3 + R_3 \parallel R_4} \cdot \frac{R_3}{R_3 + R_4} \right)$$

$$i_{R_3} = \frac{V_A}{R_3} ; \quad V_A = -i \times R_2 = -\frac{v_{in}}{R_1} \times R_2$$

bilancio di correnti in A:  $i_{R_4} = i - i_{R_3} = \frac{v_{in}}{R_1} + \frac{v_{in} R_2}{R_1 R_3}$

$$v_{out} = V_A + i_{R_4} \times R_4 = -\frac{v_{in} R_2}{R_3} - \frac{R_4}{R_3} \frac{v_{in} R_2}{R_1} - \frac{v_{in} R_4}{R_1} =$$

$$= -v_{in} \left[ \frac{R_2}{R_3} + \frac{R_4}{R_3} \frac{R_2}{R_1} + \frac{R_4}{R_1} \right] = -v_{in} \frac{R_2}{R_3} \left[ 1 + \frac{R_4}{R_3} + \frac{R_4}{R_2} \right]$$

$$\Downarrow G_{id} = -\frac{R_2}{R_1} \left[ 1 + \frac{R_4}{R_3} + \frac{R_4}{R_2} \right] = -\frac{1M\Omega}{1M\Omega} \left[ 1 + \frac{1M\Omega}{200k} + \frac{1M\Omega}{1M\Omega} \right] =$$

$$= -7$$

$$G_{reale} = \frac{G_{id}}{1 - \frac{1}{G_{loop}}} = \frac{-7}{1 + \frac{1}{7700}} = -6.999$$

Calcolo  $G_{loop}$ :  $G_{loop} = -\frac{R_3 \parallel (R_2 + R_4)}{R_4 + [R_3 \parallel (R_2 + R_4)]} \cdot \frac{R_1}{R_1 + R_2} A_o =$

$$= -A_o \frac{\frac{(R_2 + R_4) \cdot R_3}{R_2 + R_4 + R_3}}{R_4 + \frac{(R_2 + R_4) \cdot R_3}{R_2 + R_4 + R_3}} \cdot \frac{R_1}{R_1 + R_2} = -A_o \frac{R_1 R_3}{R_4 (R_2 + R_1 + R_3) + (R_2 + R_4)}$$

$$= -\frac{A_o R_1 R_3}{(R_2 + R_4)(R_3 + R_4) + R_3 R_4} = -A_o \frac{R_1}{R_1 + R_2 + R_3 \parallel R_4} \cdot \frac{R_3}{R_3 + R_4} =$$

$$= -10^5 \times \frac{1M\Omega}{1M\Omega + 1M\Omega + \frac{1M\Omega \parallel 200k}{107k}} \cdot \frac{200k}{200k + 1M\Omega} = -10^5 \times 0.45 \times 0.167$$

$$= -0.077 \cdot 10^5 =$$

$$= -7.7 \cdot 10^3$$

②  $R_{in}|_{id} = R_1 + 0 \Rightarrow R_{in} = R_1 + \frac{R_{eq}}{1 - G_{loop}}$

$$R_{eq} = (R_3 + R_3 \parallel R_4) \parallel R_{in} = 1.167M\Omega \parallel 500k\Omega = 350k\Omega$$

$$G_{loop}^* = -A_o \frac{R_{i0}}{R_{i0} + R_2 + R_3 \parallel R_4} \cdot \frac{R_3}{R_3 + R_4} =$$

$$= -10^5 \frac{500k}{500k + 1M\Omega + 167k} \cdot \frac{200k}{1.2M\Omega} = -0.05 \cdot 10^{-5} = -5000$$

↓

$$R_{in} = R_1 + \frac{350k\Omega}{1 + 5000} = 1M\Omega + 70\Omega \approx 1M\Omega$$


Rispetto ad una configurazione invertente standard posso avere elevato impedenza di ingresso, senza compromessi messi sul guadagno.

③

$$R_{comp} = R_1 \parallel [R_2 + R_3 \parallel R_4] = 1M\Omega \parallel [1M\Omega + \frac{200k \parallel 1M\Omega}{167k}] =$$

$$= 538.5k\Omega$$

④

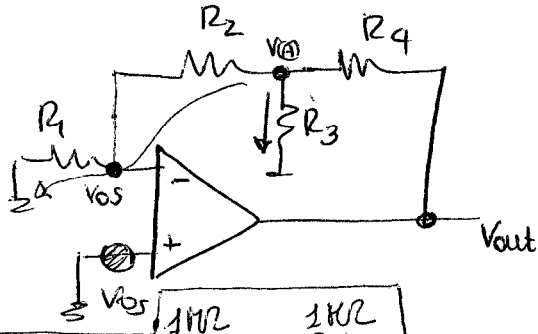

$$V_A = \pm V_{os} + \pm \frac{V_{os}}{R_1} \cdot R_2$$

$$i_{R_3} = \frac{V_A}{R_3} = \pm \frac{V_{os}}{R_3} \left(1 + \frac{R_2}{R_1}\right)$$


$$i_{R_4} = i_{R_3} + \pm \frac{V_{os}}{R_4} = \pm \frac{V_{os}}{R_3} \left(1 + \frac{R_2}{R_1}\right) \pm \frac{V_{os}}{R_4}$$

$$V_{out}|_{os} = V_A + i_{R_4} \cdot R_4 = \pm V_{os} \left[ \left(1 + \frac{R_2}{R_1}\right) + \frac{R_4}{R_3} \left(1 + \frac{R_2}{R_1}\right) + \frac{R_4}{R_4} \right] =$$

$$= \pm 5mV \times 13 = \pm 65mV$$

$$V_{out}|_{os} = \pm V_{os} \cdot \left[ \frac{R_4 + R_3}{R_3} \right] =$$
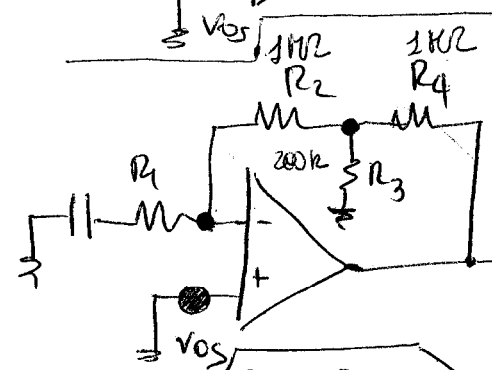
$$= \pm 5mV \cdot \left[ \frac{1.2M\Omega}{200k} \right] = \pm 30mV$$



$$V_{out}|_{os} = \pm V_{os} \left[ 1 + \frac{R_2 + R_4}{R_1} \right] =$$

$$= \pm 5mV \left[ 1 + \frac{2M\Omega}{1M\Omega} \right] = \pm 15mV$$