

①  $V^+ = \frac{R_5}{R_4 + R_5} V_{in}$        $V^- = V^+$  per c.c.t.o circuito virtuale


Poiché l'opamp è ideale in  $R_3$  non passa corrente  $\Rightarrow V_A = V^-$

$$V_{out} = i \cdot (R_1 + R_2) = \frac{V^-}{R_1} (R_1 + R_2) = \frac{R_5}{R_4 + R_5} \cdot \left(1 + \frac{R_2}{R_1}\right) V_{in}$$

La resistenza  $R_L$  non influisce sul guadagno ideale

$$\downarrow G_{id} = \frac{V_{out}}{V_{in}} = \frac{R_5}{R_4 + R_5} \left(1 + \frac{R_2}{R_1}\right) = \frac{50}{50 + 50} \left(1 + \frac{100k}{10k}\right) = +5.5$$
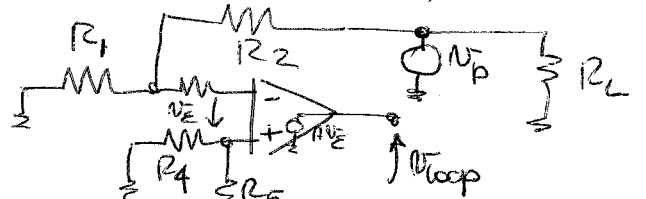
$$G_{reale} = \frac{G_{id}}{1 - \frac{1}{G_{loop}}}$$




$$G_{loop} = \frac{-R_1}{R_1 + R_2} \cdot A = -\frac{10k}{10k + 100k} \cdot 10 = -$$

$$= -9.1 \cdot 10^4$$

$$\downarrow G_{reale} = \frac{5.5}{1 + \frac{1}{9.1 \cdot 10^4}} = +5.4999$$

②

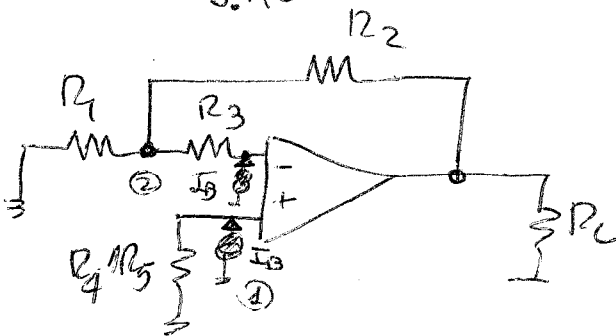

$$V_{out}^{(1)} = I_B \cdot R_4 \parallel R_5 \cdot \left(1 + \frac{R_2}{R_1}\right) = 1\mu A \cdot 50 \parallel 50 \cdot \left(1 + \frac{100k}{10k}\right) =$$

$$= 1\mu A \cdot 25\Omega \cdot 11 = 2.75 \cdot 10^{-4} V = 0.275 mV$$

$$V_{out}^{(2)}: V_A = -I_B \cdot R_3 \Rightarrow I_{R1} = \frac{V_A}{R_1} = -I_B \frac{R_3}{R_1}$$

$$I_{R2} = I_B + I_B \frac{R_3}{R_1} = I_B \left(1 + \frac{R_3}{R_1}\right)$$

$$V_{out}^{(2)} = V_A - I_{R2} \cdot R_2 = -I_B \cdot R_3 - I_B \cdot \left(1 + \frac{R_3}{R_1}\right) \cdot R_2 =$$


$$= -I_B \left[ R_3 + R_2 \left(1 + \frac{R_3}{R_1}\right) \right] = 1\mu A \left[ 220\Omega + 100k \left(1 + \frac{220\Omega}{10k}\right) \right]$$

③ Per compensare le correnti di bias:

$$R_{comp} + R_4 \parallel R_5 = R_3 + R_1 \parallel R_2$$

$$\Downarrow R_{comp} = R_3 + R_1 \parallel R_2 - R_4 \parallel R_5 = 220 \Omega + 10k \parallel 100k - 25 \Omega = 9.295 k\Omega$$

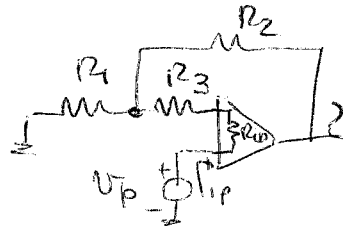④  $R^* \parallel i_d = \infty \Rightarrow R^* = R_o^* (1 - G_{loop}^*)$




$$R_o^* = R_{id} + R_3 + R_1 \parallel R_2 = 1M\Omega + 220 \Omega + 10k \parallel 100k = 1.009 M\Omega$$

$$G_{loop}^* = \frac{-R_1 \parallel (R_3 + R_{id})}{R_2 + R_1 \parallel (R_3 + R_{id})} \quad A_o = \frac{-10k \parallel (220 \Omega + 1M\Omega)}{100k + 10k \parallel (220 \Omega + 1M\Omega)} * 10^6 = 9$$

$$\Downarrow R^* = 1.009 M\Omega * (1 + 9 * 10^4) = 90.8 G\Omega$$

⑤  $CMRR = 50 \text{ dB} = 316$

$$50 \text{ dB} = 20 \log CMRR$$

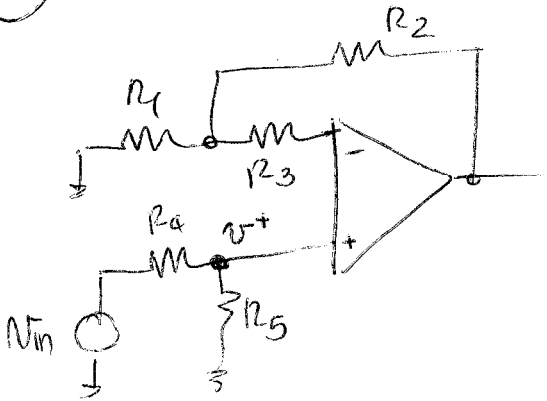


$$V^- = \frac{R_5}{R_4 + R_5} \cdot V_{in}$$

$$V_{cm}^- = \frac{V_+ + V_-}{2}$$

$V_- \approx V_+$  (nelle hp di  $A_{dm} \rightarrow \infty$ , poiché  $R_3$  non scorre corrente)
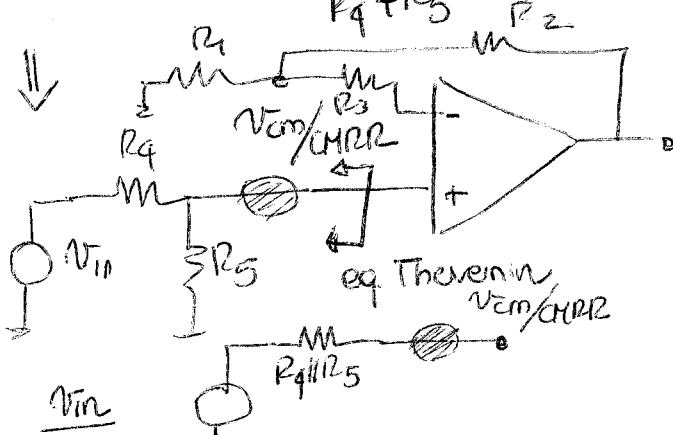
$$\Downarrow V_{cm}^- = \frac{R_5}{R_4 + R_5} V_{in}$$



$$V_{out} = \left[ \frac{V_{in}}{2} \pm \frac{V_{cm}}{CMRR} \right] * \left( 1 + \frac{R_2}{R_1} \right) =$$

$$= \left[ \frac{150 \text{ mV}}{2} \pm \frac{150 \text{ mV}}{2} \cdot \frac{1}{316} \right] * \left( 1 + \frac{100k}{10k} \right) =$$

$$= \begin{matrix} + \\ - \end{matrix} 0.828 \text{ V} \text{ invece di } 0.825 \text{ V}$$

⑥ Errore statico di guadagno

$$\varepsilon = \left| \frac{G_{id} - G_{reale}}{G_{reale}} \right| = \left| \frac{G_{id} - \frac{G_{id}}{1 - 1/G_{loop}(s)}}{G_{id}/(1 + 1/G_{loop}(s))} \right| =$$

$$= \left| 1 - \frac{1}{1 - 1/G_{loop}(s)} \right| = \left| 1 - \frac{-1}{G_{loop}(s)} \right| = \frac{1}{|G_{loop}(s)|} = 1.1 \cdot 10^{-5}$$

⇓  
 $\varepsilon\% = 1.1 \cdot 10^{-3} \%$

⑦  $I_{out} = \frac{V_{out}}{R_L} + \frac{V_{out}}{R_1 + R_2}$  (nel caso di opamp ideale)


⇓  
 $V_{out}|_{max} = I_{out} / \left( \frac{1}{R_L} + \frac{1}{R_1 + R_2} \right) = 10mA / \left( \frac{1}{500\Omega} + \frac{1}{110k\Omega} \right) =$   
 $= 10mA * 498\Omega = 4.98V$

⑧  $SR = 0.75V/\mu s$

$$\left. \frac{dV_{out}}{dt} \right|_{MAX} = A_{in} * G * \omega * \cos \omega t|_{max} = A_{in} * G * \omega$$

⇓  
 $A_{in}|_{MAX} = \frac{SR}{G\omega} = \frac{0.75V/\mu s}{\frac{1}{2} * 11 * 2 * \pi * 15kHz} = 1.45V$

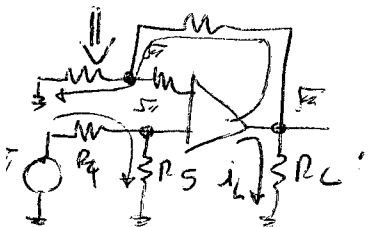⑨  $V_{in} = 200mV \Rightarrow V_{out} = V_{in} * \frac{R_5}{R_4 + R_5} \left( 1 + \frac{R_2}{R_1} \right) = \frac{V_{in}}{2} * 11 =$   
 $= 1.1V$



$$I_L = \frac{V_{out}}{R_L} = \frac{1.1V}{500\Omega} = 2.2mA$$