
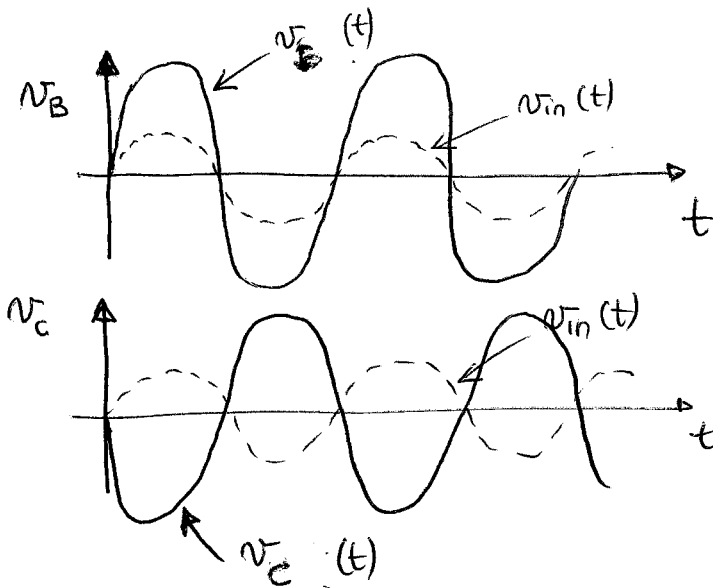


$$\textcircled{1} \quad v_B(t) = v_{in}(t) * \left(1 + \frac{R_2}{R_1}\right) = v_{in}(t) * \left(1 + \frac{15k}{10k}\right) = \frac{5}{2} v_{in}(t)$$
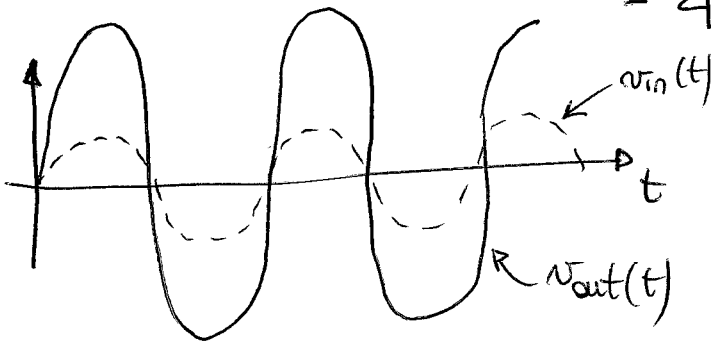
$$v_C(t) = v_{in}(t) * \left(-\frac{R_2}{R_1}\right) = -1.5 v_{in}(t)$$



$$\Downarrow \quad v_{out}(t) = v_B(t) - v_C(t) = 2.5 v_{in}(t) - (-1.5 v_{in}(t)) = 4 v_{in}(t)$$



$$\textcircled{2} \quad G_{ideale} = \frac{v_{out}}{v_{in}} \Big|_{ideale} = +4$$

Per calcolare G_{reale} deve calcolare G_{loop} per ciascuno dei due op amp. $A_0 = 90dB = 10^{\frac{90}{20}} = 3$

$$G_{loop} = -\frac{R_1}{R_1 + R_2} * A_0 = -\frac{10k}{10k + 15k} * 3.2 \cdot 10^4 = -12800$$


$$\Downarrow \quad G_{reale|_C} = \frac{G_{idC}}{1 - \frac{1}{G_{loop}}} = \frac{-1.5}{1 + \frac{1}{12800}} = -1.4999$$

$$G_{reale|_B} = \frac{G_{idB}}{1 - \frac{1}{G_{loop}}} = \frac{+2.5}{1 + \frac{1}{12800}} = 2.4998$$

} $G_{reale} = 3.999$
 cioè G_{ideale}
 perché G_{loop} è molto alto.

③ Poiché sia v_B che v_C possiamo saturare a $\pm 14V$, la massima ampiezza della sinusoide di uscita sarà di $28V$

④

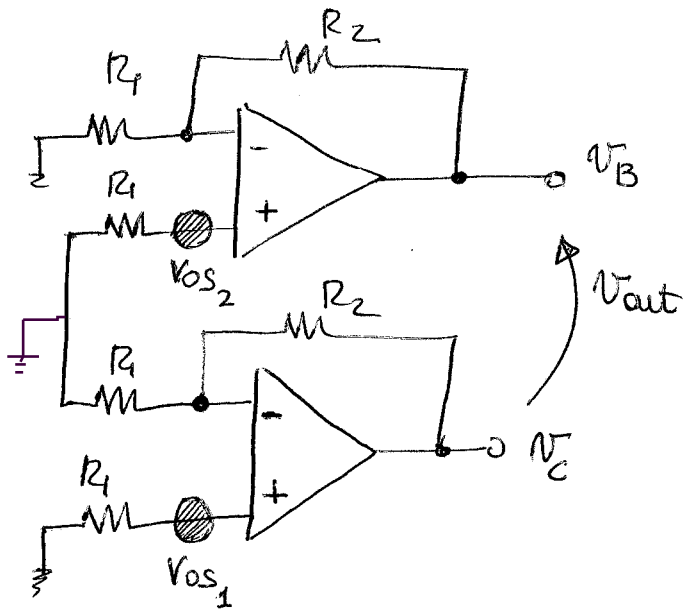

$$v_b = \pm V_{os2} \left(1 + \frac{R_2}{R_1} \right)$$

$$v_c = \pm V_{os1} \left(1 + \frac{R_2}{R_1} \right)$$

⇓

$$v_{out} = v_b - v_c = \pm V_{os2} \left(1 + \frac{R_2}{R_1} \right) \mp V_{os1} \left(1 + \frac{R_2}{R_1} \right) = \pm 2 \cdot 5mV \cdot \left(1 + \frac{15k}{10k} \right) = \pm 25mV$$