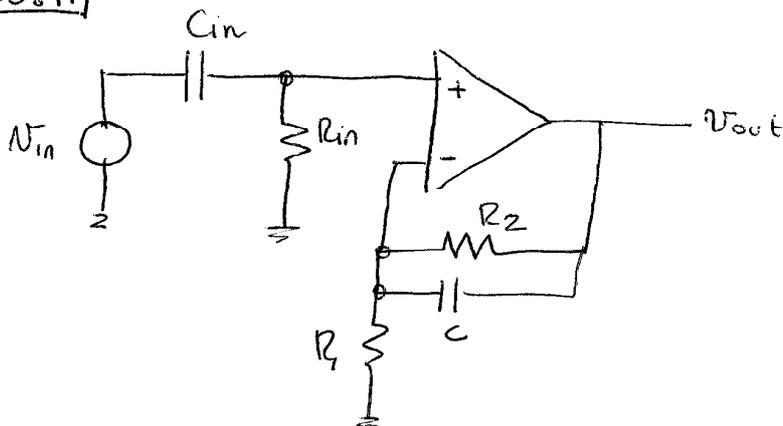


2^o PROVA - RECUPERO

ES. A




1.

$$\begin{aligned}
 G_{ideale}(s) &= \frac{R_{in}}{R_{in} + \frac{1}{sC_{in}}} \cdot \left(1 + \frac{R_2}{R_1} \cdot \frac{1}{1 + sCR_2} \right) = \\
 &= \frac{sC_{in}R_{in}}{1 + sC_{in}R_{in}} \cdot \left(\frac{(1 + sCR_2)R_1 + R_2}{R_1(1 + sCR_2)} \right) = \\
 &= \frac{sC_{in}R_{in}}{1 + sC_{in}R_{in}} \cdot \frac{R_1 + R_2}{R_1} \cdot \frac{1 + sC \frac{R_2R_1}{R_1 + R_2}}{1 + sCR_2} = \\
 &= \left(1 + \frac{R_2}{R_1} \right) \cdot \frac{sC_{in}R_{in}}{1 + sC_{in}R_{in}} \cdot \frac{1 + sCR_{||}}{1 + sCR_2}
 \end{aligned}$$

$$\begin{aligned}
 f_{in} &= 3.41 \\
 \uparrow \\
 \tau_{in} &= C_{in}R_{in} = 47\text{ms} \\
 \tau_2 &= CR_2 = 47\mu\text{s} \quad \hookrightarrow f_2 = 3.4 \\
 \tau_2 &= CR_{||} = 23.5\mu\text{s} \\
 \hookrightarrow f_2 &= 6.8
 \end{aligned}$$


2.

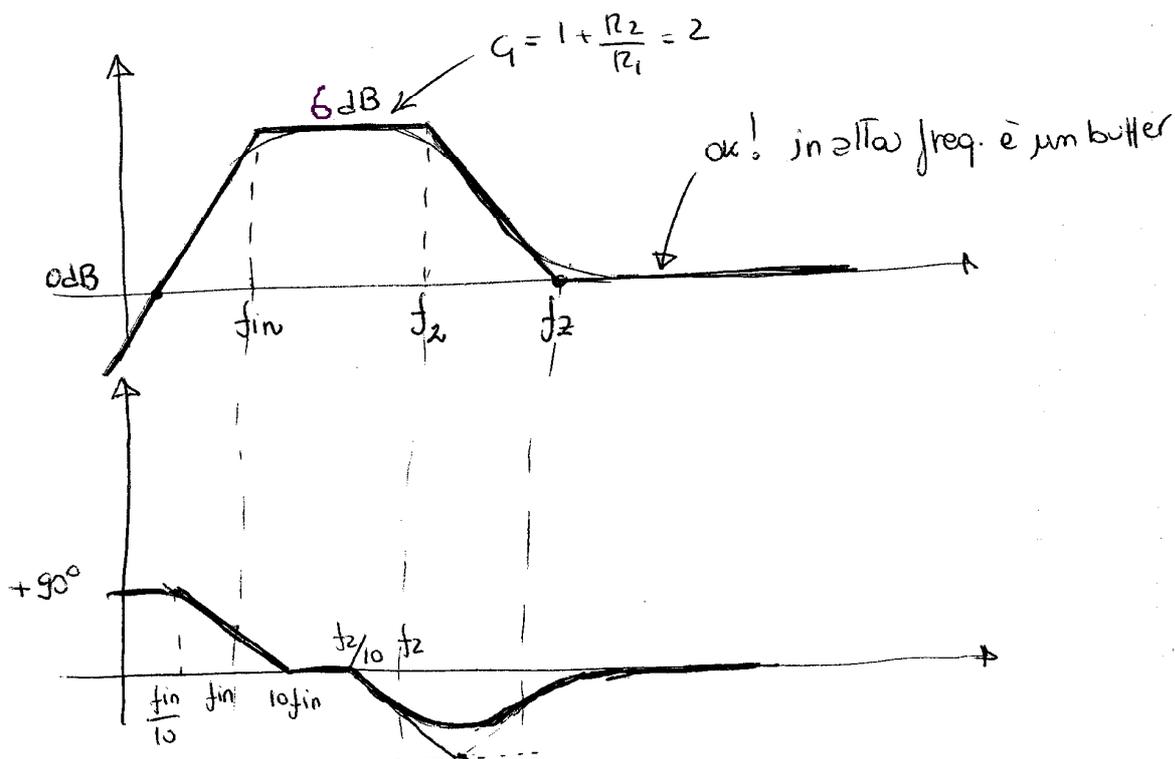


3. $f_{in} = 100 \text{ Hz} \Rightarrow$ centro banda

$$V_{out} = \left(1 + \frac{R_2}{R_1}\right) \cdot V_{in} \sin(2\pi f_{in} t) = +200 \text{ mV} \sin(2\pi f_{in} t)$$

4.

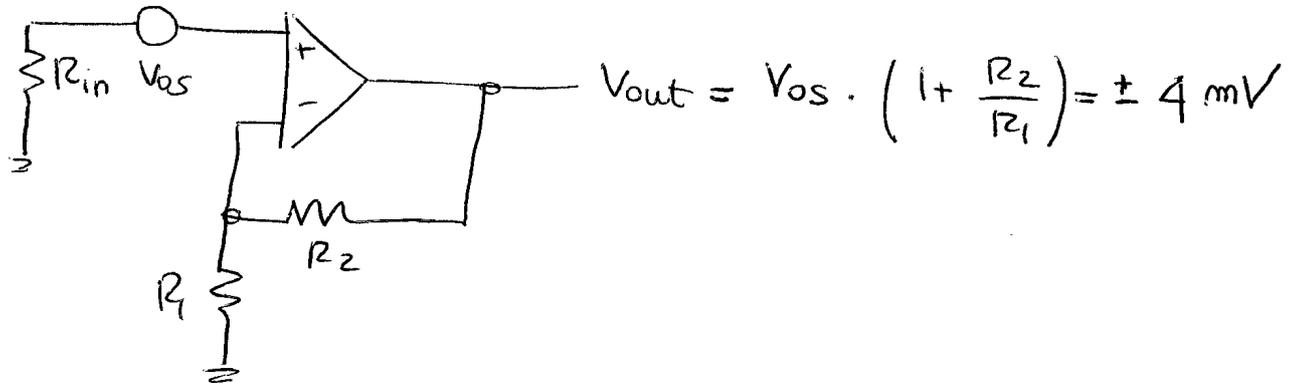

5.

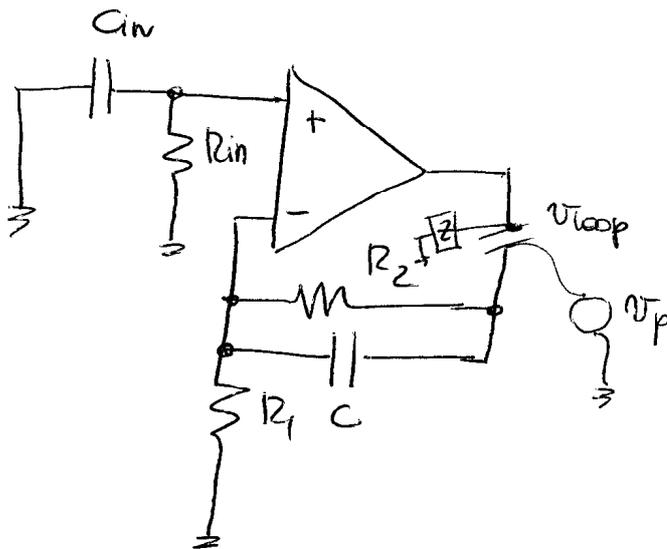


$$G_{loop} = \frac{V_{loop}}{V_p} = - \frac{R_1}{R_1 + \frac{R_2}{1+sCR_2}} \frac{A_0}{1+s\tau_0} =$$


$$A_0 = 100 \text{ dB} = 10^5 \Rightarrow f_0 = \frac{G_{PWP}}{A_0} = \frac{10^7 \text{ Hz}}{10^5} = 10^2 \text{ Hz} = 100 \text{ Hz}$$

$$\hookrightarrow \tau_0 = 1.6 \text{ ms}$$
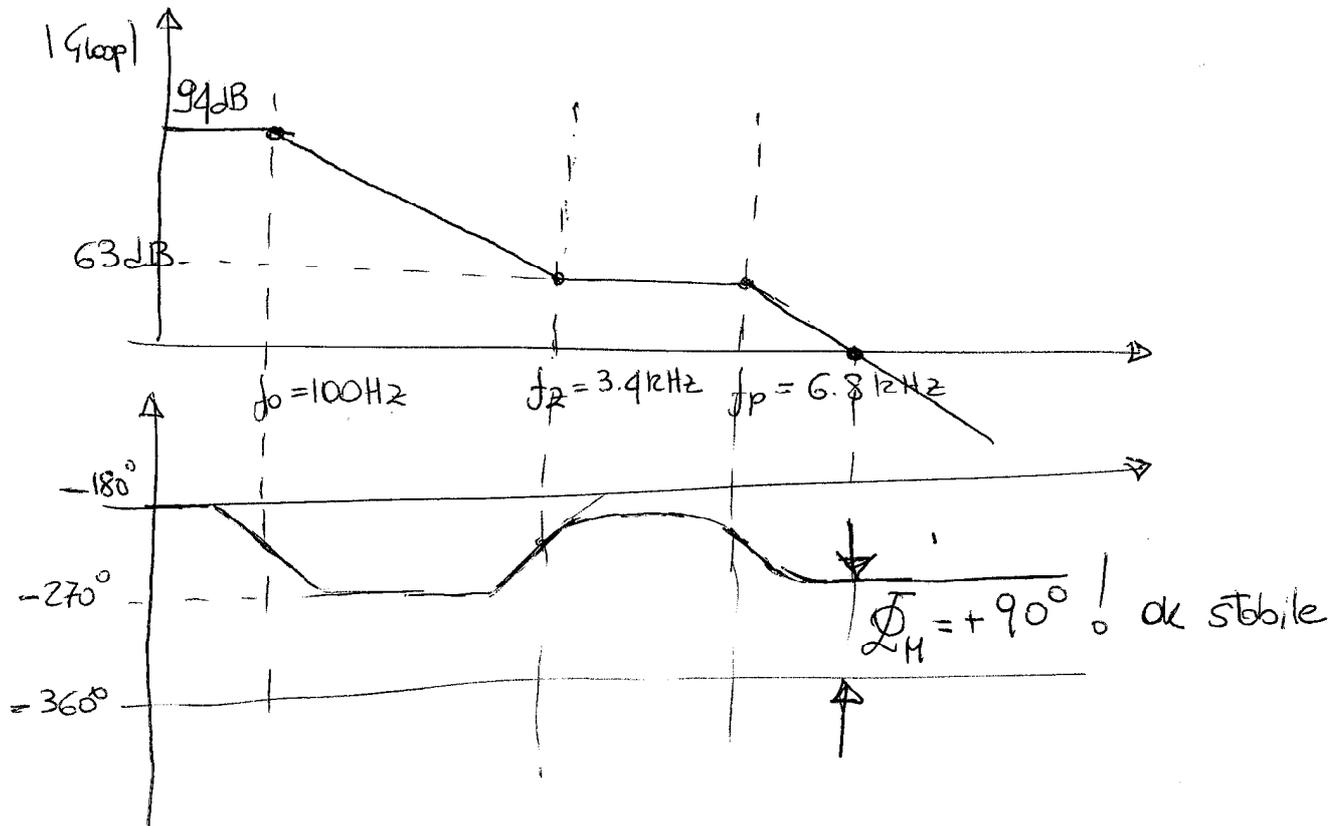
$$= - \frac{R_1}{R_1 + R_2} \frac{1 + sCR_2}{1 + sCR_{//}} \frac{A_0}{1 + s\tau_0} = 5 \cdot 10^4 \frac{1 + s\tau_2}{1 + s\tau_p}$$



6.

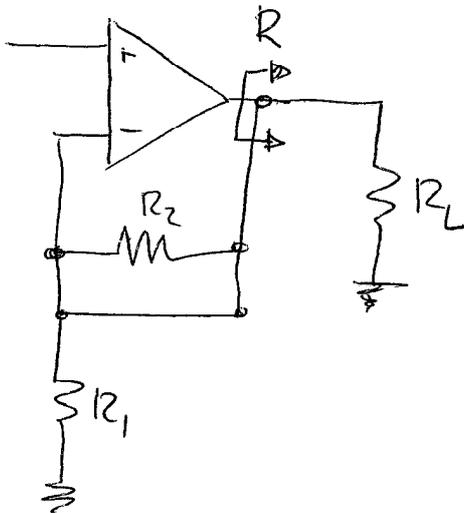

$$R = R_L // R_2 = 10 \text{ k}\Omega // 10 \text{ k}\Omega = 5 \text{ k}\Omega$$

$$I_{\text{picco}} = \frac{V_{\text{picco}}}{R} = \frac{5 \text{ V}}{5 \text{ k}\Omega} = 1 \text{ mA}$$

ES. B

$$1. \quad V_{in} \Big|_{\text{ADC}} = V_{in} \cdot \left(1 + \frac{90 \text{ k}\Omega}{10 \text{ k}\Omega}\right) = 10 V_{in} \Rightarrow V_{in} \Big|_{\text{ADC}} \Big|_{\text{MAX}} = 3 \text{ V}$$

non copre l'intero dinamico dell'ADC

$$\Downarrow$$

$$\frac{5 \text{ V}}{2^m} = 1 \text{ mV} \Rightarrow \frac{5 \text{ V}}{2^m} = 10^{-3} \text{ V} \Rightarrow 2^m = 5000$$

$$\hookrightarrow m = 12.3 \Rightarrow \boxed{13 \text{ bit}}$$

$$2. \quad T_{\text{SAMP}} = T_S + T_H = 5 \mu\text{s} \Rightarrow f_{\text{SAMP}} = 2 f_{\text{MAX}} \text{ per Teo. compio}$$

$$f_{\text{MAX}} = \frac{f_{\text{SAMP}}}{2} = \frac{1}{2 T_{\text{SAMP}}} = \frac{1}{10 \mu\text{s}} = 100 \text{ kHz}$$

$$3. \quad \Delta V_{\text{in}} = \frac{C_{\text{stray}}}{C_{\text{stray}} + C} \cdot 5V = \frac{0.4 \text{ pF}}{0.4 \text{ pF} + 10 \text{ nF}} \cdot 5V = 0.2 \text{ mV}$$

$$1 \text{ LSB} = \frac{5V}{2^{13}} = 610 \mu\text{V}$$


$$\Delta V_{\text{ADC}} = 0.2 \text{ mV} \times 10 = 2 \text{ mV} \Rightarrow \frac{2 \text{ mV}}{610 \mu\text{V}} = 3.3 \text{ LSB}$$

$$4. \quad \frac{dv_{\text{in}}}{dt} = A_{\text{in}} \omega_{\text{in}} \cos(\omega_{\text{in}} t) \Rightarrow \left. \frac{dv_{\text{in}}}{dt} \right|_{\text{MAX}} = A_{\text{in}} \omega_{\text{in}}$$

$$\hookrightarrow \text{SR} = A_{\text{in}} \omega_{\text{in}} = 300 \cdot 10^{-3} \times 10^6 \cdot 2\pi = 1.88 \cdot 10^6 \text{ V/s} \approx 2 \text{ V}/\mu\text{s}$$

5. I_{B^+} non conta

I_{B^-} :

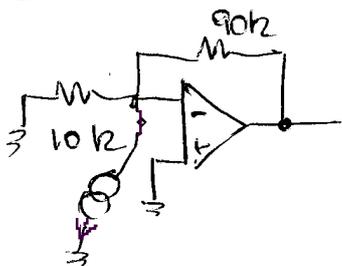

$$V_{\text{out}} = -I_{\text{B}^-} \times 90 \text{ k}\Omega = -50 \text{ nA} \times 90 \text{ k}\Omega = -4.5 \text{ mV}$$

$$\Rightarrow \text{errore statico: } \frac{4.5 \text{ mV}}{610 \mu\text{V}} = 7.4 \text{ LSB}$$