
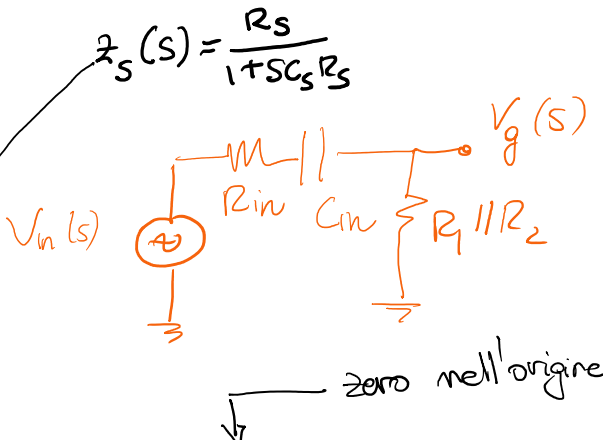


Dimensionamento capacita' di by-pass nello stadio source degenerato

Wednesday, April 7, 2021 10:42 AM

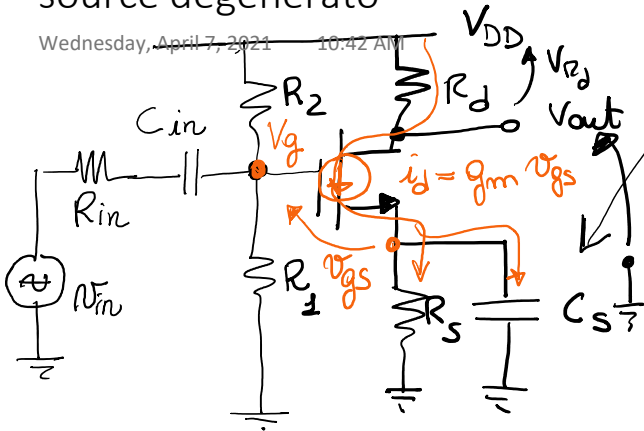


$$V_g(s) = \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_{in} + \frac{1}{sC_{gs}}} V_{in}(s)$$

$$V_{in}(s) = \frac{sC_{in} R_1 \parallel R_2}{1 + sC_{in} (R_1 \parallel R_2 + R_{in})} V_{in}(s)$$

polo con $\tau_{in} = C_{in} (R_1 \parallel R_2 + R_{in})$
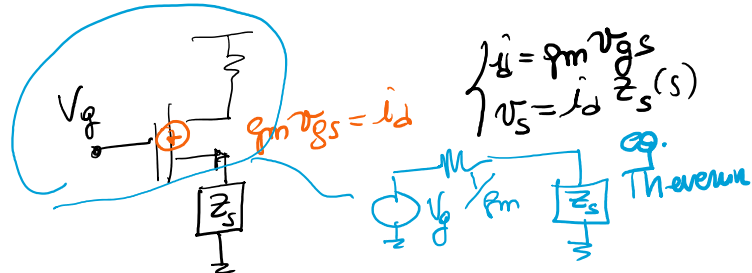
$$\hat{i}_d(s) = \frac{V_g(s)}{\frac{1}{g_m} + z_s(s)} = \frac{V_g(s)}{\frac{1}{g_m} + \frac{R_s}{1 + sC_s R_s}}$$




$$V_{out}(s) = -\hat{i}_d(s) R_d = - \frac{R_d}{\frac{1}{g_m} + \frac{R_s}{1 + sC_s R_s}} \cdot \frac{sC_{in} R_1 \parallel R_2}{1 + sC_{in} (R_{in} + R_1 \parallel R_2)} V_{in}(s)$$

$$= - \frac{g_m R_d (1 + sC_s R_s)}{1 + sC_s R_s + g_m R_s} \cdot \frac{sC_{in} R_1 \parallel R_2}{1 + sC_{in} (R_{in} + R_1 \parallel R_2)} V_{in}(s)$$

FUNZIONE DI TRASFERIMENTO

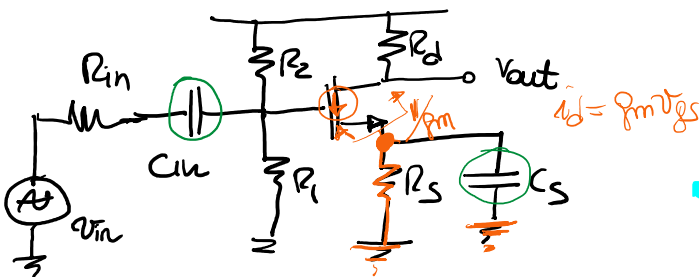
$$T(s) \triangleq \frac{V_{out}(s)}{V_{in}(s)} = - \frac{g_m R_d}{(1 + g_m R_s)} \cdot \frac{1 + sC_s R_s}{1 + sC_s \frac{R_s}{1 + g_m R_s}} \cdot \frac{sC_{in} R_1 \parallel R_2}{1 + sC_{in} (R_{in} + R_1 \parallel R_2)} =$$



$$= - \frac{g_m R_d}{1 + sC_s (R_s \parallel \frac{1}{g_m})} \cdot \frac{sC_{in} R_1 \parallel R_2}{1 + sC_{in} (R_{in} + R_1 \parallel R_2)}$$

$$= - \frac{g_m R_d}{1 + g_m R_S} \cdot \frac{1 + s C_S R_S}{1 + s C_S (R_S \parallel \frac{1}{g_m})} \cdot \frac{1}{1 + s C_{in} (R_{in} + R_S \parallel R_2)}$$

Medio - Alta frequenza

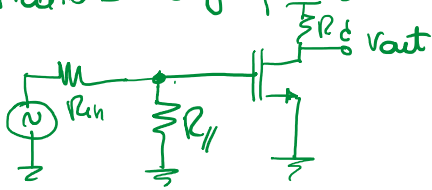

$$G_{MF} = \frac{R_{11}}{R_{in} + R_{11}} \cdot (-g_m R_d)$$

$$Z_S(s) = \frac{R_S}{1 + s C_S R_S} \rightarrow \infty \text{ sse } s = -\frac{1}{C_S R_S}$$

- 1 polo con $\tau_p = C_S (R_S \parallel \frac{1}{g_m})$
- 1 zero con $\tau_z = C_S R_S$ ($\tau_p < \tau_z$)

- partizione in ingresso
- zero nell'origine
 - polo con $\tau_{in} = C_{in} (R_{in} + R_S \parallel R_2)$

Avere uno zero nello $F_d T$ significa che $\exists \bar{s}$ t.c. $\forall V_{in}(\bar{s}) \neq 0$
 $V_{out}(\bar{s}) = 0$

$$|T(j\omega)|_{dB}$$

