

PAROLA DIGITALE


$D = [b_{N-1}, b_{N-2}, \dots, b_2, b_1, b_0]$ Parola digitale a N bit

$D = b_0 \cdot 2^0 + b_1 \cdot 2^1 + b_2 \cdot 2^2 + \dots + b_{N-2} \cdot 2^{N-2} + b_{N-1} \cdot 2^{N-1}$

BIT MENO SIGNIFICATIVO
LEAST SIGNIFICANT BIT
LSB

BIT PIU' SIGNIFICATIVO
MOST SIGNIFICANT BIT
MSB

INVERTER CMOS

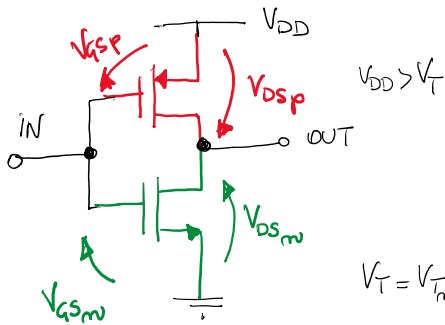

PMOS : $\begin{cases} V_{gs_p} = iN - V_{DD} \\ V_{ds_p} = V_{out} - V_{DD} \end{cases}$



mMOS : $\begin{cases} V_{gs_m} = iN \\ V_{ds_m} = OUT \end{cases}$

$V_T = V_{Tm} = |V_{Tp}|$

$iN = V_{DD}$



$V_{gs_m} = V_{DD} > V_{Tm} \Rightarrow$ mMOS acceso

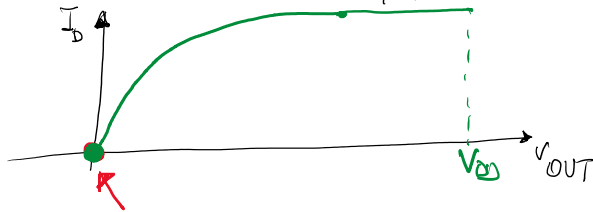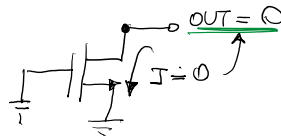$V_{gs_p} = V_{DD} - V_{DD} = 0 \Rightarrow$ pMOS off
 $V_{gs_m} = V_{DD}$



$iN = 0$


$V_{gs_m} = 0$

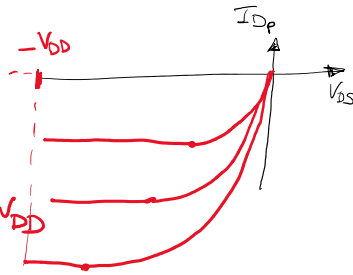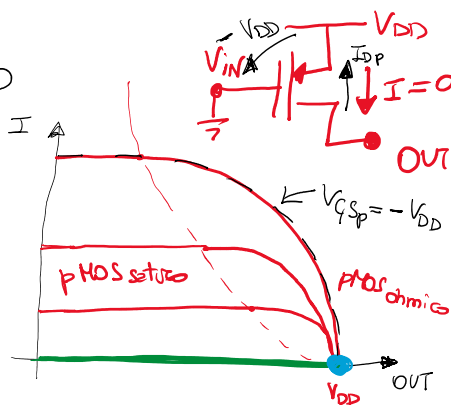


$V_{ds_p} = OUT - V_{DD}$

$V_{ds_p} = 0 \Rightarrow OUT = V_{DD}$


$V_{ds_p} = V_{DD} \Rightarrow OUT = 0$

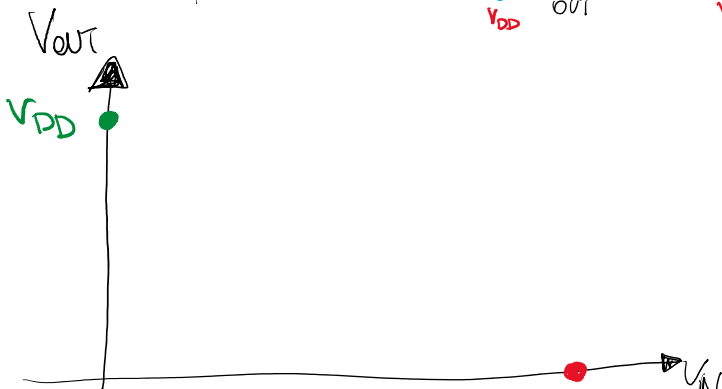

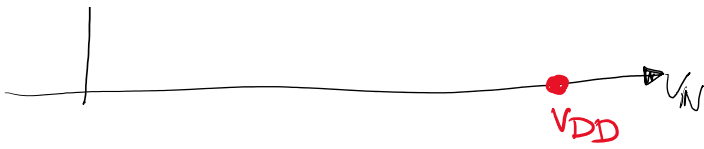

SOLUZIONE

ESERCIZIO

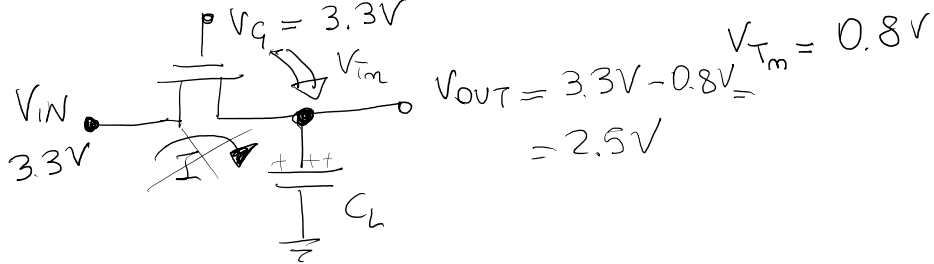

a) $V_{IN} = 0V$

lato ingresso $V_G - V_{in} = 3.3V \Rightarrow$ c'è canale \Rightarrow MOS acceso
 ma in cond. stazionaria $I = 0 \Rightarrow V_{DS_m} = 0 \Rightarrow V_{out} = V_{in} = 0V$

b) $V_{IN} = 3.3V$

lato ingresso $V_G - V_{in} = 0V \Rightarrow$ non c'è canale
 ma lato uscita se $V_{out} = 0V \Rightarrow V_G - V_{out} = 3.3V > V_{T_m}$
 c'è canale lato uscita, MOS on