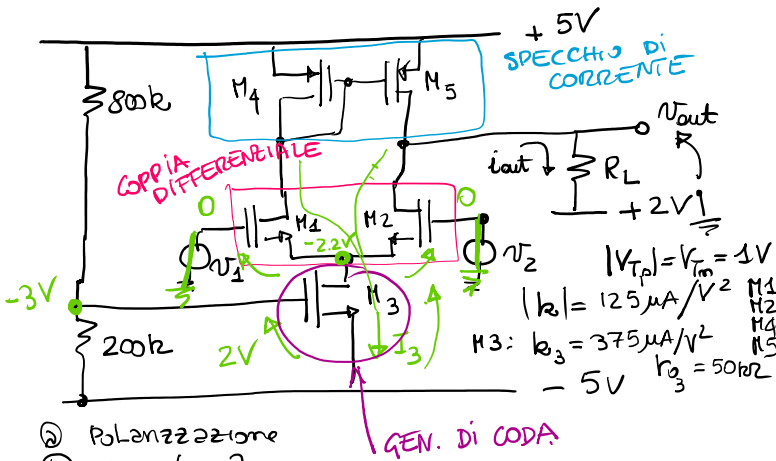


**ESERCIZIO : STADIO DIFFERENZIALE CON CARICO A SPECCHIO**



- a) Polarizzazione
- b)  $i_{out}/v_d$ ?
- c)  $i_{out}/v_{cm}$ ?

2) POLARIZZAZIONE  
tip MOS satuti

$$V_{GS3} = -5V + \frac{200k}{(200+800)k} [5V - (-5V)] = -3V$$

Trascuro  $r_{o3}$  (salvo verificare che  $I_{r_{o3}} \ll I_{M3}$ )

$$I_3 = k_3 (V_{GS3} - V_{Tn})^2 = 375 \mu A$$


$$I_1 = I_2 = \frac{I_3}{2} = 187.5 \mu A$$

$$I_1 = I_2 = k_1 (V_{GS1} - V_{Tn})^2$$

$$V_{GS1} = V_{GS2} = V_{GS} = V_{Tn} + \sqrt{\frac{I_1}{k_1}} = V_{Tn} + \sqrt{\frac{187.5 \mu A}{125 \mu A/V^2}} = 2.2V$$

$$I_{r_{o3}} = \frac{-2.2V - (-5V)}{r_{o3}} = 56 \mu A !!$$

Polarizzazione iterativa

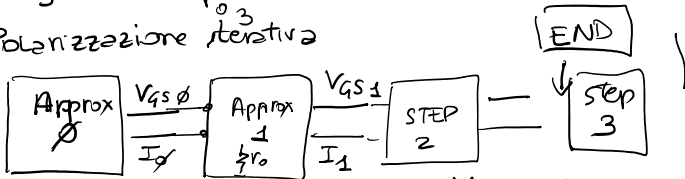

$$\frac{V_{GS_m} - V_{GS_{m-1}}}{V_{GS_m}} \text{ piccolo \%$$

$$I_{d1} = I_{d2} = \frac{I_3}{2} + \frac{I_{r_{o3}}}{2} = \frac{375 \mu A + 56 \mu A}{2} = 215.5 \mu A$$

$$V_{GS1} = V_{Tn} + \sqrt{\frac{215.5 \mu A}{125 \mu A/V^2}} = 2.31V$$

$$V_{DS3} = -2.31V - (-5V) = 2.7V$$

$$I_{r_{o3}} = \frac{V_{DS3}}{r_{o3}} = 54 \mu A \quad (56 \mu A)$$

|| ...

$$\underline{\underline{3.6\%}}$$


$$\hookrightarrow I_{r_{o3}} = \frac{V_{D3}}{r_{o3}} = 54 \mu A \quad (3.6\%)$$

OK

$$I_{M3TOT} = 375 \mu A + 54 \mu A$$

$$I_1 = I_2 = \frac{I_{M3TOT}}{2}$$


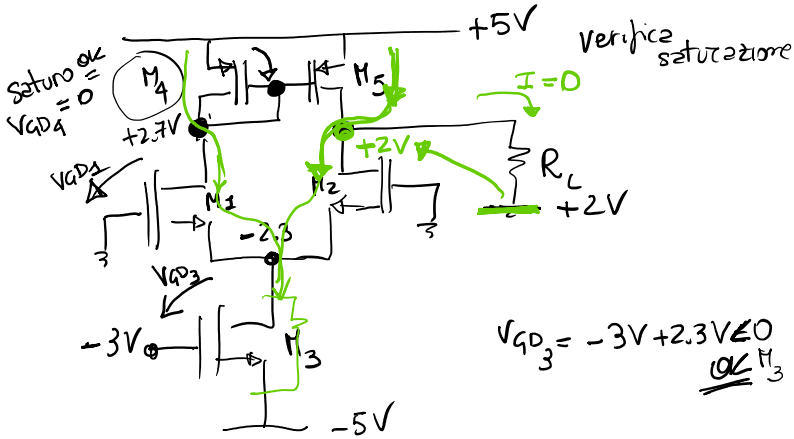
$$g_{m1} = g_{m2} = 328 \mu A/V \quad g_m = 2k(V_{GS} - V_{Tn})$$



$$V_{GD3} = -3V + 2.3V = -0.7V < 0 \quad \text{OK } M_3$$

$$V_{GD1} = -2.7V < 0 < V_{Tn} \quad \text{OK } M_1$$

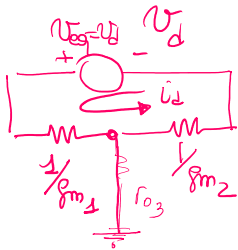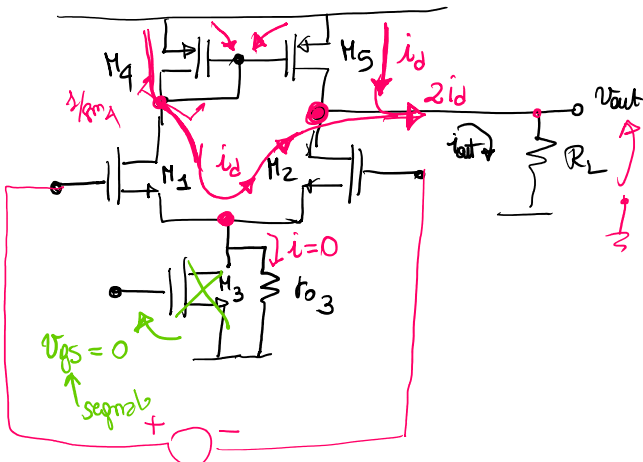b) Comportamento su segnale differenziale



$$i_d = \frac{V_d}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}}$$


$$i_{out} = 2i_d \Rightarrow v_{out} = 2i_d R_L = \frac{2 V_d R_L}{\frac{2}{g_m}}$$

$$G_{diff} = \frac{v_{out}}{V_d} = g_m R_L = 328 \mu A/V \times 10k\Omega = +3.28$$

c) Analisi su segnale di modo comune




② analisi su segnale di modo comune -

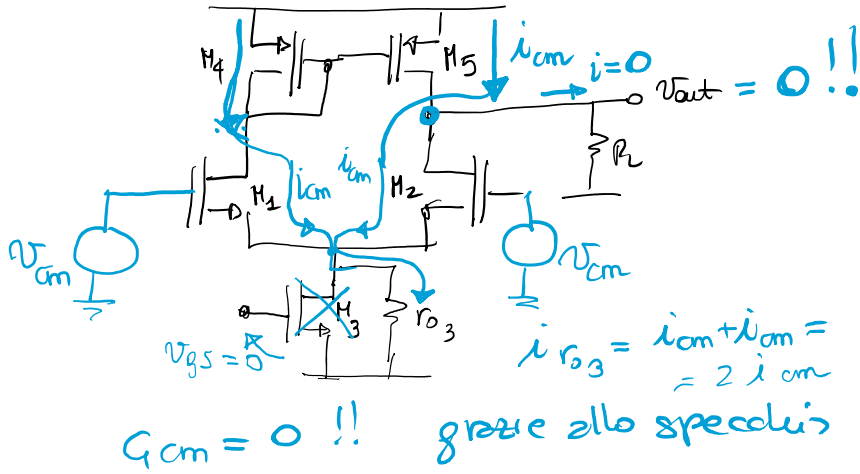

④  $M_4$  e  $M_5$  con  $r_o$   $|V_A| = 25V$

$$r_{o4} = r_{o5} = \frac{|V_A|}{I_4} = \frac{25V}{215.5\mu A} = 116k\Omega$$

• guaiolo differenziale

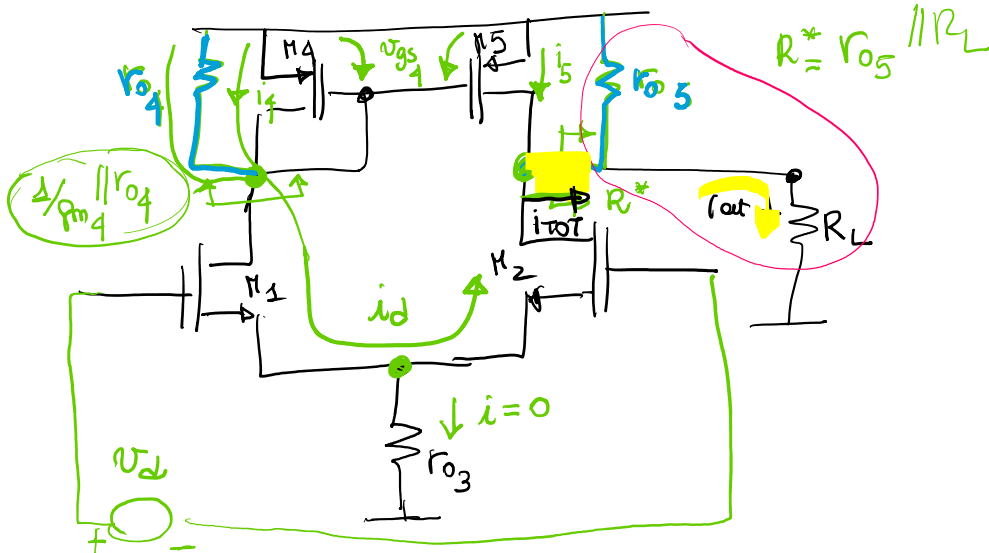

$$i_5 = i_4$$

$$i_4 \neq i_d \quad i_d = i_4 + i_{r_{o4}}$$

$$i_4 = \frac{r_{o4}}{1/g_{m4} + r_{o4}} i_d$$

partitore di corrente tra  $1/g_{m4}$  e  $r_{o4}$

$$v_{gs4} = -i_d \left( \frac{1}{g_{m4}} \parallel r_{o4} \right)$$

$$v_{gs5} = v_{gs4} \Rightarrow i_{d5} = g_{m5} v_{gs5} = g_{m5} v_{gs4} = g_{m5} \left[ -i_d \left( \frac{1}{g_{m4}} \parallel r_{o4} \right) \right]$$

$$i_5 = -i_{d5} \quad |$$

$r_{o5} \quad i$

$$i_5 = -i_{d5}$$

$$i_{TOT} = i_d + i_5 = i_d + i_4 = i_d \left[ 1 + \frac{r_{o4}}{\frac{1}{g_{m4}} + r_{o4}} \right]$$

→ 2 per  $r_{o4} \rightarrow \infty$

$$i_{out} = \frac{r_{o5}}{r_{o5} + R_L} i_{TOT}$$


$$v_{out} = i_{out} R_L \parallel r_{o5}$$

$$A_{v_{diff}} = \frac{v_{out}}{v_d} = \frac{R_L \parallel r_{o5}}{A\beta_d} \left[ 1 + \frac{r_{o4}}{\frac{1}{g_{m4}} + r_{o4}} \right]^*$$

$$* \frac{v_d}{\frac{1}{g_{m3}} + \frac{1}{g_{m2}}} =$$

$$= (R_L \parallel r_{o5}) \left[ 1 + \frac{r_{o4}}{\frac{1}{g_{m4}} + r_{o4}} \right] \frac{g_m}{2}$$

• modo comune

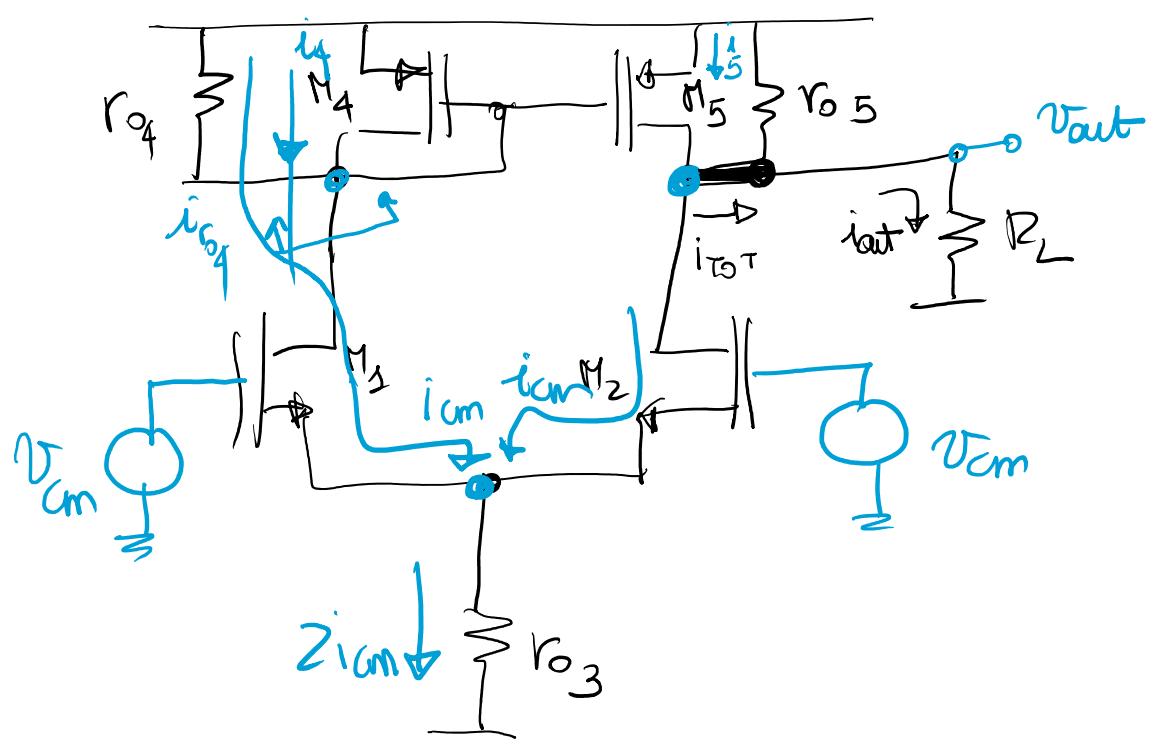

$$i_5 = i_4 = i_{cm} \frac{r_{o4}}{r_{o4} + \frac{1}{g_{m4}}}$$

$$V_{out} = \hat{i}_{TOT} * (r_{o5} \parallel R_L)$$

$$\hat{i}_{TOT} \neq i_{cm} = \hat{i}_5$$

$$\hat{i}_{TOT} = \hat{i}_5 - i_{cm}$$

$$V_{out} = \underline{(r_{o5} \parallel R_L)} \left[ i_{cm} \frac{r_{o4}}{r_{o4} + \frac{1}{g_{m4}}} - i_{cm} \right]$$

$r_{o4} \rightarrow \infty \rightarrow 1$

$$g_{cm} \neq 0$$

$$g_{cm} = -2.25 \cdot 10^{-3}$$

$$g_{diff} = 2.98$$

$$\left. \begin{array}{l} g_{cm} = -2.25 \cdot 10^{-3} \\ g_{diff} = 2.98 \end{array} \right\} CMRR = \left| \frac{g_{diff}}{g_{cm}} \right| =$$

$$= 1300 \Rightarrow \sim 60 \text{ dB}$$